

A M A T E U R R A D I O

FEBRUARY 1963

1st February, 1963

An Invitation

Dear Fellow Amateur,

Through your magazine I issue to you an invitation to participate in the National Field Day Contest on the 9th and 10th February, 1963.

You may perhaps not be able to place a station in the field, obviously you have certain obligations. However may I ask that during this Contest you at least operate your home rig. By so doing you will help all contestants.

The W.J.A. holds very few Contests, so you should at least be able to participate in one during the year. Please make it the National Field Day.

Yours faithfully,

"The Spirit of Amateur Radio."

R.S.V.P.

By calling on any band
on the 9th & 10th Feb.



Vol. 31, No. 2



TRANSISTOR POWER SUPPLY

A. & R. Type PS25, 45 watts output,
To Clear £17/10/0 incl. tax
A. & R. Type PS21, 60 watts output,
To Clear £22/10/0 incl. tax

LSG11 SIGNAL GENERATOR

120 Kc.-390 Mc.
Freq. range (six
bands): 120 Kc. to
120 Mc. on funda-
mentals; 120 to 390
Mc. on harmonics.
Mod. freq. 400 and
1,000 c.p.s. Tubes:
12BH7, 6AR5. Rec-
tifier: half wave
selenium. Provision
for crystal os-
cillator (x'tal not
supplied), 1 to 15
Mc. 100, 117 or
230v. a.c. input, 50/60 c.p.s. Size: 7½ x 10½ x
4½ in. Weight: 6 lb.



Price: LSG11—£16/17/6 inc. tax

PLUGS AND SOCKETS

Jones' small 6-pin Plug and Socket
..... 7/6 pair
2-pin Mike Plugs and Sockets, 4/6 pair
Phone Plug (with 2 ft. Cord) and Jack,
Brand new 2/6 set

CO-AXIAL CABLE

50 ohm, UR67, 3/8" diam., in 25 yd.
Rolls 30/-; or 1/6 yard.
52 ohm UR43, 3/16" diam., in 12 yd.
Rolls 15/-; or 1/6 yard.
72 ohm UR70, 3/16" diam., in 27 yd.
Rolls 30/-; or 1/6 yard.

METERS

0-500 μ A. (scaled 0-600v, No. 128 Type)
1½" hole, 1½" round case, new, 30/- ea.
0-50 mA., 3¼" round, 2½" hole, brand
new 30/- ea.

POWER TRANSFORMERS

150-0-150v., 30 mA., c.t. 6.3v., 1.7a. 32/6
225v.-0-225v., 50 mA., 6.3v., 2a., £2
250v.-0-250v., 60 mA., 6.3v. 1a., 6.3v.
c.t. 2a. £2/10/0

SPECIALS

200H Multimeter £5/12/6
VCR97 type C.R.T. Sockets, bakelite,
New 10/- each
EF50 Valve and Ceramic Socket 6/6
EA50 Valve Sockets 1/6
Left/Right Indicators, Type 1, with
shunt 200 μ A., less shunt 100 μ A., 25/-
Type "S" Time Delay Relay, 10-second,
2R7540, 30-volt 30/-
Ceramic Shaft Couplings 3/6
Pointer Knobs, small (black or wh.), 1/6
Belling Lee Coaxial Plugs and Sockets,
suit 1" coax. 3/6 socket, 4/- plug
Crystal Earphone (suit Transistor
Radio) 5/6

Call Books 6/-, Log Books 5/6, post ext.

NEW VALVES

1A3	2/6	10	4	£1	7E6	3/6	7	a	£1
1A5	5/-	5	a	£1	7S7	7/6	3	a	£1
1C7	3/-	7	a	£1	7W7	2/6	10	a	£1
1D5GT	5/-	5	a	£1	12A6	4/-	6	a	£1
1D8	7/6	3	a	£1	12AH7	5/-	5	a	£1
1H4	5/-	5	a	£1	12AT7	15/-			
1H5	5/-	5	a	£1	12AU7	15/-			
1H6	5/-	5	a	£1	12C8	5/-			
1K4	5/-	5	a	£1	12H6	3/6			
1K5	5/-	5	a	£1	12J5	5/-	5	a	£1
1LN5 (CV781)					12SA7GT	10/-			
	5/-	5	a	£1	12SC7	5/-	5	a	£1
1M5G	5/-	5	a	£1	12SK7	5/-	5	a	£1
1P5	2/-	10	a	£1	12SQ7	5/-			
1Q5	5/-	5	a	£1	12SR7	5/-	5	a	£1
1S4	7/6	3	a	£1	14A7	3/6	7	a	£1
1S5	10/-				16Z5	5/-	5	a	£1
1T4	5/-	5	a	£1	16Z6	5/-	5	a	£1
2A5	7/6				16Z9	5/-	5	a	£1
2A6	7/6				30	1/3			
2D21	15/-				35T	30/-			
2X2	5/-	5	a	£1	71A7	7/6	3	a	£1
3A4	10/-				80	13/-			
3A5	10/-				807	7/6	3	a	£1
3AP1	25/-				808	10/-			
3BP1	35/-				809	20/-			
5U4GB	14/6				815	15/-			
5V4G	15/-				830H	15/-			
5Y3GT	15/9				832A	19/6			
5Z5	17/6				866	5/-	5	a	£1
6A3	7/6	3	a	£1	954	5/-	5	a	£1
6AG7	12/6				955	5/-	5	a	£1
6AJ5	7/6	3	a	£1	956	5/-	5	a	£1
6AM5 (EL91)	10/-				958A	2/6	10	a	£1
6AM6 (EF91)	10/-				2051	5/-			
6B7	10/-				5763	22/-			
6BE6	15/-				AV11	2/11			
6C4	5/-	5	a	£1	DL75	2/6	10	a	£1
6C5	5/-	5	a	£1	EA50	2/-	10	a	£1
6C8	10/-				EC91/6AQ4	10/-			
6CH6	2/-				ECC35	20/-			
6D6	5/-	5	a	£1	ECH33	20/-			
6F5	7/6				EF36	5/-	5	a	£1
6F6	12/6				EF39	5/-	5	a	£1
6F8	5/-				EF50	3/6			
6H6 Metal	3/6				EF70	5/-	5	a	£1
6J6	10/-				EF72	5/-	5	a	£1
6K7	5/-	5	a	£1	EF73	5/-	5	a	£1
6K8G	20/-				EL41	10/-			
6K8GT	12/6				EF91	5/-			
6L7	5/-	5	a	£1	KT61 (6V6)	15/-			
6SA7	7/6				QOE03/12	47/6			
6SC7	7/6				QOE04/20	£3½			
6SF5	7/6	3	a	£1	QQV06/40	97/6			
6SH7	4/-	5	a	£1	RL18	7/6	3	a	£1
6SJ7	12/6				UL41	7/6	3	a	£1
6SN7	12/6				VR53	5/-	5	a	£1
6SS7	7/6	3	a	£1	VR101	5/-	5	a	£1
6T7	7/6	3	a	£1	VR102	5/-	5	a	£1
6V4	11/4				VR103	5/-	5	a	£1
6V6GT	16/-				VR105	10/-			
6X5	15/-				VR136	2/-	12	a	£1
6Y6	5/-	5	a	£1	VR137	2/6			
7A8	2/-	11	a	£1	VT25	5/-			
7C5	5/-	5	a	£1	VT78	3/6			
7C7	2/-	12	a	£1	VT127	4/11	5	a	£1
					VT501	7/6	3	a	£1

CONDENSERS—1/- each

Ceramic

22 pF. 500 volt 100 pF. 500 volt
33 pF. 500 volt 470 pF. 500 volt

Metalpak

0.1 μ F. 650v. d.c. 0.05 μ F. 500v. d.c.
0.1 μ F. 175v. d.c. 0.02 μ F. 750v. d.c.
0.5 μ F. 500v. d.c.

Electrolytic

32 μ F. 350 volt, 8/- each

TECH MULTIMETER



300 μ A. movement.
AC and DC voltages:
0-10, 0-50, 0-250, 0-500,
0-1000v.
Current ranges (mA.):
0-1, 0-100, 0-500 mA.
Ohms range: 0-100,000
ohms.
Size: 3¼ x 2½ x 1¼
inches.
Complete with leads.

Price only £3/1/0, post paid.

AMERICAN POTENTIOMETERS

American Bradley, 2" long, ¼" shaft,
1" diam. Available in following sizes:
20,000, 25,000, 30,000, 50,000, 100,000,
250,000 ohms, ½, 1 and 2 megohms.

Price 2/6 each

OA79 DIODES

Well known make. Brand New.

To Clear—2/6 each

TRANSISTOR POWER SUPPLIES

A. & R. Types PS21 and PS25.
Prices on Application.

CRYSTAL MICROPHONES

Price only

57/6



Stand to suit
15/- extra.

Model BM3 (illustrated): Response 100-8,000 c/s,
fitted with 6 ft. cable and phone plug with on-
off switch. Can be used on stand for hand use.

BM3 Insert 10/- each
Piezo LM3, lapel type 25/-
Piezo HM7, hand type w/plug, 35/-
Piezo SM1, hand type w/plug, 27/6
Piezo DX29, Dynamic Mike, pencil type
with stand £4/2/6

5.5 Mc. VIDEO COILS

Contains slug-tuned coil former.
6d. each

1N21 SILICON DIODES

U.h.f. mixer, design freq. 3,060 Mc.
7/6 each, or 3 for £1.

HAM RADIO SUPPLIERS

5A MELVILLE STREET, HAWTHORN, VICTORIA

Phone 86-6465

North Balwyn tram passes corner. Money Orders and Postal Notes payable North Hawthorn P.O. 5/- Packing Charge.

"AMATEUR RADIO"

JOURNAL OF THE WIRELESS INSTITUTE OF AUSTRALIA. FOUNDED 1910.

FEBRUARY 1963

Vol. 31, No. 2

Editor:

K. M. COCKING VK3ZFQ

Publications Committee:

G. W. Bate (Secretary) VK3AOM
S. T. Clark VK3ASC
R. S. Fisher VK3OM
R. W. Higginbotham VK3RN
E. C. Manifold VK3EM

Advertising Enquiries:

C/o P.O. Box 36, East Melbourne, C.2, Vic.
OR
Mrs. BELLAIRS, Phone 41-3535, 478 Victoria
Parade, East Melbourne, C.2, Victoria. Hours
10 a.m. to 3 p.m. only.

Publishers:

VICTORIAN DIVISION W.I.A.
Reg. Office: 62a Franklin St., Melbourne, Vic.

Printers:

"RICHMOND CHRONICLE" Phone 45-2418.
Shakespeare Street, Richmond, E.1, Vic.

★

All Correspondence should be forwarded
to:-

THE EDITOR,
"AMATEUR RADIO,"
P.O. BOX 36,
EAST MELBOURNE, C.2, VIC.

before the 8th of the month preceding publication. Technical articles should preferably be typed, double spaced, on one side of the paper, signed and numbered. All drawings should be large and done in Indian ink.

★

Issued monthly on first of month. Subscription rate in Australia and Overseas is 24/- a year, in advance (post paid).

Back copies may be available; enquiries to P.O. Box 36, East Melbourne, C.2, Vic.
Any complaint regarding non delivery of "A.R." and change of address should be made to the Secretary of the member's Division and not to "A.R." direct.

★

WI Broadcasts:

VK3WI: Sundays, 1100 hours EST, simultaneously on 3573 Kc., 7146 Kc., 50.16 Mc. and 145.13 Mc.; intrastate call-backs taken on 7050 Kc. VHF 1050 hours EST on 50.16 Mc. and 145.13 Mc.; call-backs taken on 2 metres.

VK3WI: Sundays, 1030 hours EST, simultaneously on 3573 and 7146 Kc., 51.016 and 146.25 Mc. Intrastate hook-ups taken on 7135 Kc.

VK4WI: Sundays, 0900 hours EST, simultaneously on 7146 Kc. and 14.342 Mc. Intrastate hook-ups taken on 7105 Kc.

VK5WI: Sundays, 0900 SAT, on 7146 Kc. Relays on 3.7, 14.3, 50.02, 144 and 288 Mc. Intrastate hook-ups taken on 7125 Kc.

VK6WI: Sundays at 0930 hours WAST, on 7146 Kc. Intrastate hook-ups taken on 7085 Kc.

VK7WI: Sundays at 1000 hours EST, on 7146 Kc. and 3872 Kc. Intrastate hook-ups taken on 7115 Kc.

FEDERAL COMMENT

★

OLD MAN N.F.D.

Every month in the year has some special significance to the Contest-minded Amateur. October is VK-ZL month, March is A.R.R.L. DX month, December-January is Ross Hull time, and February has now become Field Day month.

Yes, the month of February is here again and to an increasing number of enthusiasts, this means dusting off the mobile or portable rig, repairing the camping equipment and migrating to that favourite hill for a day or so to participate in the National Field Day Contest.

Despite the great interest and enthusiasm shown in England and U.S.A. for Field Day events, the Contest here has never enjoyed the same popularity. Yet today, more than ever before, this Contest needs that support. With the advent of the transistor, transmitters and power supplies and even receivers make it an easier proposition than it was, say 10 years ago.

If the Amateur is to increase his stature in the eyes of the public as has been so often propounded, he must be ready and able to operate under real emergency conditions. Here is a means of achieving some practice in this type of operation and at the same time getting away from the stuffy shack.

To misquote the words of a popular song: "Tote that gear, lift that mast, you get a little fun and you land a place (we hope) in the N.F.D." So good luck in this year's Contest, the last to be held under its present title. Let's make it a bumper wind-up to the N.F.D.


FEDERAL EXECUTIVE, W.I.A.

CONTENTS

Surplus Crystal High-Frequency Filters	3	Sideband Topics:	
A Combination S.w.r. Bridge and Amplifier Linearity Indicator ..	7	288 Mc. S.s.b.	13
High Frequency Crystal Filters ..	9	KWM-1 and 40	13
More About FT241 Surplus Crystals	11	Relay Acceleration	13
National Field Day Contest, 1963, additional Rule 6A	9	Operating Procedure	13
V.h.f. Two-Way Radio for Private Aircraft	18	Federal and Divisional Monthly News Reports	20
		DX	17
		SWL	19
		VHF	15

Mullard STEREO "TEN-TEN"

WITH PRINTED CIRCUIT BOARDS

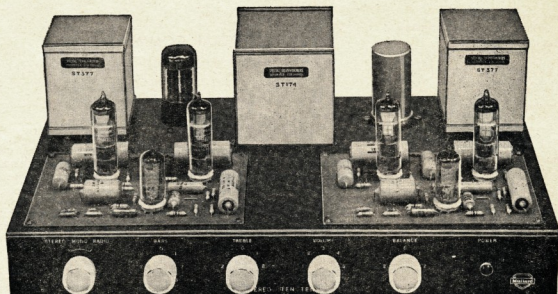


PRINTED CIRCUIT BOARD

Mullard

STEREO "TEN-TEN"

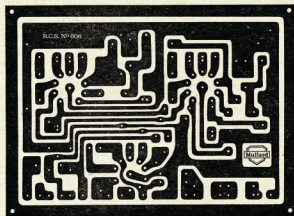High quality reproduction is achieved in this amplifier with a complement of two 6GW8/ECL86 valves and one low-noise AF pentode type EF86 in each channel, with a 5AR4/GZ34 rectifier common to both channels. The power output is 10W per channel and the performance is comparable to that of the Mullard High Quality 10W Amplifier (the well-known Mullard "Five-Ten").



MULLARD-AUSTRALIA PTY. LTD.,

35-43 CLARENCE STREET, SYDNEY, 29 2006 and

123-129 VICTORIA PARADE, COLLINGWOOD, N.S. VIC. 41 6644

Associated with MULLARD LIMITED, LONDON

The Mullard leaflet, Mullard Stereo "Ten-Ten", is available on receipt of this coupon, together with a stamped, self-addressed, foolscap envelope, from:—

Mullard-Australia Pty. Ltd. G.P.O. Box 2116, Sydney, N.S.W.
Mullard-Australia Pty. Ltd. G.P.O. Box 97, Collingwood, Vic.
and from Mullard distributors throughout the Commonwealth.

NAME.....

ADDRESS

Surplus-Crystal High-Frequency Filters*

BENJAMIN H. VESTER, W3TLN

AFTER all the recent "QST" articles on uses for high-frequency crystal filters, I've really been coveting one for a mobile s.s.b. transceiver I'm planning. The commercial price tags on filters being what they are, I decided it would have to be built from surplus crystals, or not at all. Having, during the earlier days of s.s.b., suffered with a low-frequency crystal filter (typical report was, "Gee, your voice sounds funny"), I decided to do a little reading before dragging out the soldering iron this time.

An article by Kosowsky¹ boils a lot of "long-hair" literature on crystal-lattice theory into a fairly simple and understandable form. One of the most interesting points to me was the fact that the crystal filter designer considers the narrow-band high-frequency crystal filter for s.s.b. to be the "easy" design—the problem getting much more exotic for the wide-band high-frequency filter. Since my buddy, W3HEC, was already tackling the tough problem of making a good low-frequency filter with the FT241 crystals, I took the easy way out and tried my hand with the high-frequency unit.

SOME BACKGROUND

If you're planning to try your hand at it, it will help if you grab a few fundamental concepts on crystal lattice filters first. The properties of the crystal itself are pretty well known, the approximate equivalent circuit being shown in Fig. 1 and the change of reactance or impedance being shown in Fig. 2. The crystal has two resonances very close together, L and C being in series resonance at f_z and L and C and Co being parallel resonant at f_p . These resonance have been given names by the network theory boys, the series resonance being called a "zero" of impedance (for obvious reasons) and the parallel resonance being called a "pole" of impedance. The symbols used for these are shown in Fig. 2.



Fig. 1.—The equivalent circuit of a crystal. L and C are the electrical equivalents of mechanical resonants in the crystal, while Co is the shunting capacitance of the electrodes and holder.

These poles and zeroes are mighty convenient little symbols for handling networks, the most convenient part being the fact that if you have a circuit with several poles and zeroes, you can often manipulate the circuit values so as to get some of the zeroes each to cancel out a pole. Hence, a circuit with a multitude of resonances (or poles and zeroes) can be arranged to have

● Using the methods and circuits outlined here, the problem of making a usable high-frequency (i.e. in the 4 to 7 Mc. range) crystal filter doesn't sound too tough, even with limited test equipment. If you've been interested in some of the newer transmitting and receiving techniques using filters in this range, here's a way to give them a whirl without a large investment.

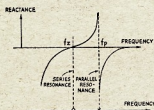


Fig. 2.—Reactance characteristics of a crystal. The series-resonant frequency, f_z , is that of L and C (Fig. 1) in series; the parallel-resonant frequency, f_p , is the resonant frequency of the parallel circuit formed by L and C in one branch and Co in the other.

its response equivalent to only a few resonances.

The universal crystal filter is a lattice circuit. The lattice is usually developed in full "four-arm" form (i.e. as a bridge circuit) and then the equivalence of the half-lattice is proved. The reader is referred to Kosowsky's article and its bibliography for the full treatment on this. We will settle for a few statements on crystal lattice filters which have been adequately proven by others.

Consider the simple one-section half lattice shown in Fig. 3. The first important point to consider is that the only way in which the lattice can give a high insertion loss between input and output is for the impedances of A and B to be about equal, so that the voltage at their common connection (point O) is equal to the voltage at the coil centre tap. Our crystals will meet the requirement pretty well if they have the same holder capacitance, so the primary problem is to build the coil so that the

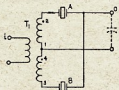


Fig. 3.—The half-lattice crystal filter. Crystals A and B should be chosen so that the parallel-resonant frequency of one is the same as the series-resonant frequency of the other. Very tight coupling between the two halves of the secondary of T1 is required for optimum results.

voltage from Terminals 1 to 2 is exactly the same as the voltage from 3 and 4. The method for realising this will be discussed a little later.

Crystals A and B are chosen to be different in frequency for the half lattice. Thus it is obvious that if we are at a zero (series resonant) frequency of, say, crystal A, the impedance balance of A and B is spoiled and there is a voltage showing up between point O and the centre of the coil. This will also occur at the pole (parallel resonant) frequency of crystal A. The same can be said for crystal B, only the unbalance is in the opposite direction. This leads us directly into the statement that the pass band of the crystal filter will be as wide as the spacing of all the poles and zeroes. This says nothing about the ripple or variation in transmission in the pass band, however, and if A and B are far apart the ripple or dip may be tremendous. Here's where the network theory boys' trick of pairing off poles and zeroes comes in handy. A little study with Fig. 2 of the way in which the impedance change around a zero differs from that around a pole will give an idea how the lattice crystals can be arranged to give a flat pass band. Fig. 4 shows the desired arrangement. The series-resonant frequency of crystal B is arranged to coincide with the parallel resonant frequency of crystal A. This will theoretically give a perfectly flat pass band from the zero of crystal A to the pole of crystal B.

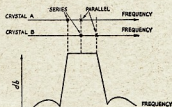


Fig. 4.—The theoretical attenuation-v.-frequency curve of a half-lattice filter shows a flat pass band between the lower series-resonant frequency and higher parallel-resonant frequency of the pair of crystals.

Our problem is now resolved down to determining the pole-zero spacing for the available crystals. The surplus FT243 crystals in the 5 Mc. range (this choice of frequency was obviously based on the excellent results being obtained with the popular HT32 transmitter) have a measured spacing of about 2.2 Kc. between their series and parallel-resonant frequencies. Thus, two of them spaced 2.2 Kc. apart in frequency are theoretically capable of giving a 4.4 Kc. bandwidth. Practically, it is very difficult to get quite this much bandwidth.

If we examine the effects that the external coupling circuitry has on the pole-zero spacing, it can be shown that both an increase and a decrease in the

* Reprinted from "QST," January, 1959.

¹ Kosowsky, "High Frequency Crystal Filter Design Techniques and Applications," Proceedings of the I.R.E., Feb., 1958.

spacing can be accomplished, by shunting inductance or capacitance, respectively, across the crystal. The most familiar example of this to most of us is in pulling a crystal oscillator's frequency by shunting a capacitor across the crystal. This technique, you will remember, only works where the crystal is being used in its parallel-resonant mode.

Referring back to Fig. 1, it is easily seen that a parallel capacitor makes Co larger and lowers the parallel-resonant frequency (pole). It will not affect the series-resonant frequency (zero), so the effect of the parallel capacitor is to move the pole closer to the zero. Similarly, it can be shown that an inductance shunted around the crystal will push the pole away from

frequency difference; best accuracy is obtained by measuring the harmonics of the generator with the receiver in the sharp crystal-filter position.[†]

Initial measurements of the two 5645 Kc. crystals I had showed a pole-to-zero spacing of 2.2 Kc. on one and 2.4 Kc. on the other. Their series-resonant frequencies were about 560 cycles apart. I decided to try these out first to get a bearing on the problem.

As indicated earlier, the push-pull coil must have very tight coupling between its two secondaries and should be chosen with a high enough inductance to avoid resonance with the crystal shunt capacitance near the pass band. I used a $\frac{3}{4}$ " ferrite toroid (origin and properties unknown) with the secondaries wound bifilar. The bifilar winding

put signal into a range which was covered by my receiver (a 75A-3) so the receiver could be used for both db. and frequency measurements. The initial response was as shown by curve "A" in Fig. 7. A 10K resistor was then added to terminate the filter and the response squared up (as shown by curve "B") to give a passable 1 Kc. high-frequency filter.

This was sufficiently encouraging, so I dug out the ammonium bifluoride[‡] etching bath from its hiding place and moved the upper-frequency crystal to a frequency 1,500 cycles above the lower frequency (W2IHW's technique for etching crystals is really simple).

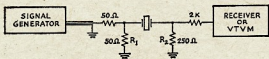


Fig. 5—Set-up for measuring the series and parallel-resonant frequencies (for pole-zero spacing) of a crystal.

the zero; unfortunately, however, this also introduces a second parallel-resonant frequency. Even the network theory boys begin to sweat a little when they begin to manipulate this many poles and zeroes in a lattice circuit, so we Hams had better avoid the complications, and shy away from trying to add tuned inductors on the input and output of the filter. If we are forced to use an inductor, we will make its inductance large enough to avoid its resonating with Co anywhere near the desired pass band.

PRELIMINARY MEASUREMENTS

Now that we have some ideas as to how crystal filters work, we will get more specific and look at the procedure by which one may be evolved. To measure the spacing between the series and parallel-resonant frequencies, we must be careful to avoid having the test circuit put shunt capacitance across the crystal and give erroneous results. The circuit in Fig. 5 was used by the writer.

To eliminate the extra shunt capacitance that a socket would add, the crystal holders were soldered directly into the circuit. The signal generator can be most any kind, so long as it has a slow tuning rate—I used one of the Command transmitters. The measurement detector can be a scope, a v.t.v.m. (with r.f. probe), or the station receiver. The low resistance R2 across it should swamp out any small amount of input capacitance it might have. If a receiver is used, a 1K or 2K resistor should probably be put in series with its input to isolate the crystal from the receiver front-end tuned circuits. The series and parallel-resonant frequencies are, of course, at the peak and null of the signal across R2. Any decent communications receiver will measure the

is illustrated in Fig. 6. The enclosed LS series coils made by C.T.C. probably would work just as well. (It would probably be very difficult to get tight enough coupling with air-wound coils, however.) I arbitrarily made each half of the secondary coil with an inductance of 50 microhenrys; this required 25 bifilar turns, or 50 turns total. The exact inductance is not at all crucial—the important thing is the tight coupling.

EXPERIMENTAL RESULTS

A filter was constructed with the circuit shown in Fig. 3. It was fed from a low impedance and its output was into a 6AK5 mixer grid. The mixer grid effectively shunting some capacitance across the crystals. This mixer was used to beat the filter out-

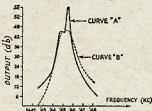


Fig. 7—Measured attenuation curves of a half-lattice filter using two nominal 5645 Kc. crystals having series-resonant frequencies separated by 560 cycles. A—without resistance termination; B—with 10,000 ohm terminating resistor. In taking the data for these curves and those shown in Figs. 8, 9, and 11, the attenuation was based on the manufacturer's calibration of the receiver used in the tests.

i.e., after adjusting the generator to the series-resonant frequency, let the generator allow and shift the receiver to some higher range where a generator harmonic can be heard and its frequency measured. Then shift back to the fundamental frequency, adjust the generator to the parallel-resonant frequency, shift the receiver again and then measure the generator harmonic adjacent to the first one. The frequency separation between the crystals is of course equal to the frequency difference between the harmonics divided by the order of the harmonic. This method usually will give improved accuracy only if the receiver calibration can be read to the same accuracy—e.g., 1 kc. per db. division on the harmonic range as on the fundamental.—Editor.

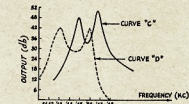


Fig. 8—Attenuation curves of half-lattice filter with crystals of the same nominal frequency as in Fig. 7, but with 1.5 Kc. separation. C—with 0.5 megohm terminating resistor; D—shunt coil added across the output to resonate with capacitance present at that point.

The initial results with this were anything but encouraging. Curve "C" in Fig. 8 illustrates the results. It was obvious that the capacitance across the lattice output had shoved the poles too close to the zeroes, or else the 0.5 meg terminating resistor was improper. I tried tuning the capacitance out with a slug-tuning coil and got all kinds of interesting results (curve "D" in Fig. 8 is typical), none of them usable. When I terminated the filter with lower values of resistance, however, the results improved markedly. With just the right resistor, 1.5K in this case, the pass band was flat over a reasonable width. Curve "E" in Fig. 9 shows the final results. The bandwidth is just barely great enough for phone use.

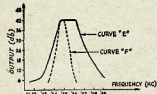


Fig. 9—E-half-lattice filter using same crystals as in Fig. 8, but with 1,500 ohm terminating resistor. F—using two nominal 5645 Kc. crystals separated 300 cycles, with 3,900 ohm terminating resistor.

Since I had one other 5645 Kc. crystal which was 300 cycles from one of the original crystals, I substituted it in and got curve "F" in Fig. 9. This time a 3.9 K terminating resistor gave the flattest pass band.

If greater rejection off the skirts is required, there are several ways in which these sections can be cascaded. Crystals of the same frequency can be paralleled on the half-lattice arms, or an isolating tube can be placed between



Fig. 6—Bifilar winding on a toroidal core.

[†]Newland, "A Safe Method for Etching Crystals," "QST," January 1958.

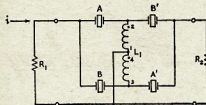


Fig. 10.—Half-lattice filters cascaded in a back-to-back arrangement. The theoretical curve of such a filter has increased skirt selectivity and fewer spurious responses, as compared with a simple half lattice, but the same pass band as the simple circuit.

two sections. A simpler technique is to connect them back to back as shown in Fig. 10. This method of connection will minimise spurious off-frequency response since the probability of getting the spurious responses of crystals A and B to line up with those of crystals A1 and B1 is pretty small. The coil, L1, is again wound bifilar and R1 and R2 are chosen experimentally for the best pass band. The crystals should be matched as closely as you can read their frequency—this is pretty easy with the etching technique.

Fig. 11 shows the response I got from four 7300 Kc. crystals, connected like Fig. 10 (crystals A and A1 were 1.5 Kc. higher than B and B1). The same bifilar coil was used. Incidentally, I got a peep inside one of the 9 Mc. commercial s.s.b. filters recently and they used this circuit. Their filter used an LS-9 coil (C.T.C. Corp.) for L1.

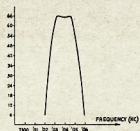


Fig. 11.—Attenuation curve of filter using four nominal 7300 Kc. crystals, pairs separated 1.5 Kc. in the circuit of Fig. 10.

I measured the spacing between series and parallel resonance of a few of the other surplus crystals that were lying around and got the following results:—

Crystal Freq.	Type	Pole-Zero Spacing
8725 Kc.	FT243	2.7 Kc.
7250 Kc.	FT243	2.3 Kc.
7380 Kc.	Plated-surplus	5 Kc.
7010 Kc.	Plated surplus	6 Kc.
8900 Kc.	Plated-harmonic cut	20 Kc.

Obviously, the plated crystals will give wider-band filters.

If you're interested in an asymmetrical filter which has a gradual fall-off on one side, then the circuit shown in Fig. 12 can be used. Here both the crystals are on exactly the same frequency. The coils are again bifilar and C is tuned to give the desired pass band. The potential bandwidth here is only half that obtained with the half-lattice. It should work nicely with the plated crystals, however.

I hope this will encourage some of you fellows to try your hand at build-

ing filters. I only have a handful of crystals and have only spent a couple of weeks playing with them, so I have not had an opportunity to try all the circuits. ●


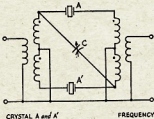


Fig. 12.—An asymmetrical filter and theoretical attenuation curve.

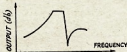

TECHNICAL ARTICLES

Readers are requested to submit articles for publication in "A.R.," in particular constructional articles, photographs of stations and gear, together with articles suitable for beginners, are required.



Manuscripts should preferably be typewritten but if handwritten please double space the writing. Drawings will be done by "A.R." staff provided that the article is illustrated.



Photographs will be returned if the sender's name and address is shown on the back of each photograph submitted.



Please address all articles to the
EDITOR "A.R."
P.O. BOX 36,
EAST MELBOURNE, C.2,
VICTORIA.

Wireless Institute of Australia

The Institute was founded in 1910 to promote interest in Amateur Radio. Today each State has its own Division, responsible for intrastate matters.

Any person with an interest in Amateur Radio, including Short Wave Listening, may join the Institute; it is not necessary to possess a transmitting license.

Enquiries for membership should be made to the Secretary in the respective State; addresses are as follows:—

New South Wales: 14 Atchison Street, Crows Nest.
Victoria: P.O. Box 36, East Melbourne, C.2.
Queensland: Box 638J, G.P.O., Brisbane.
South Australia: Box 1234K, G.P.O., Adelaide.
Western Australia: Box N1002, G.P.O., Perth.
Tasmania: Box 851J, G.P.O., Hobart.

The W.I.A. also provides various aides for Amateurs and these are available from the Victorian Division, or other State offices.

STATION LOG BOOK OR S.W.L. LOG

Size 10" x 8", with 96 pages ruled to provide all essential requirements for Amateur Stations or Short Wave Listeners. Available for 5/6 plus postage.

LOG SHEETS

Specially ruled sheets for Field Day or Portable Station operation. Basically as the Log Book above, but includes requirements for the Federal Contest Committee. Available for 2/6 for fifty sheets, plus postage.

AUSTRALIAN RADIO AMATEUR CALL BOOK

The only directory of all registered Australian Amateur Radio Stations and Short Wave Listeners. Contains current details of Australian B.C. and T.V. Stations, plus a DX Countries List, Prefixes and Zones. Also lists all QSL Bureau addresses. Issued yearly and available for 6/- each.

"AMATEUR RADIO" MAGAZINE


The only hobby magazine devoted entirely to Amateur Radio, Short Wave Listening, news, views, and construction articles. Available on direct subscription from the Victorian Division for 24/- a year post free.



INVITE YOUR FRIENDS TO JOIN THE W.I.A. TODAY . . . and become one of the members. Remember that you receive a free copy of "A.R." with your subscription.

Famous "TRAP MASTER" Aerials

by **Mosley**

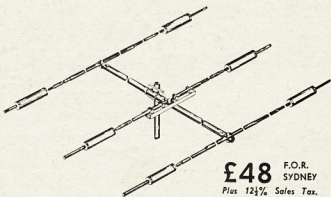

£48 F.O.R.
SYDNEY
Plus 12½% Sales Tax.

Model TA-33-JR (illustrated) is a three-band trap type rotary beam aerial designed to function with equal efficiency on 10, 15 and 20 metre bands. No mechanical switching is needed nor are tuning devices of any sort required. If your rig is capable of working into a 52 ohm load, simply connect a single 52 ohm coax line between transmitter and aerial, tune transmitter to any one of the three bands and sit back to enjoy the finest DX and the most satisfyingly solid contacts of your Ham career!

With proper installation, your TA-33-JR will provide up to 8 db. forward gain over a reference dipole and will offer 25 db. front-to-back ratio. The TA-33-JR will handle up to 300 watts input to the final amplifier at 100% amplitude modulation.

WORK 3 BANDS - 10, 15 & 20 - EQUALLY WELL with "TRAP MASTER"

... DX AERIALS of WORLD RENOWN!

Australian Agents: MAURICE CHAPMAN and CO. PTY. LTD., 158 Clarence Street, Sydney. BX 5127

VOLTAGE REGULATION!




TRIMAX

for Transformers
and associated equipment

...with the TRIMAX

60 V.A. and 250 V.A. VOLTAGE REGULATORS which are available with flexible lead entries and 3-pin socket or with conduct entries.

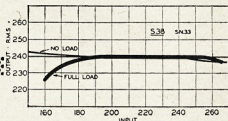

LM 25

L M ERICSSON-TRIMAX PTY. LTD.

CNR. WILLIAMS ROAD AND CHARLES STREET, NORTH COBURG, VIC. . . PHONE 35 1203

A Combination S.W.R. Bridge and Amplifier Linearity Indicator*

H. C. SHERROD, W5ZG

AN s.w.r. indicator/relative power output indicator is a useful device which is popular because of its simplicity and economy. The usual unit consists of an r.f. sampling device connected in the transmission line and a high resistance d.c. voltmeter. The sampled voltages are rectified to reveal the forward and reflected powers in the line. From this information we can determine the standing wave ratio in the usual manner and the relative power output is indicated by the forward reading.

THE LINEARITY MEASUREMENT

It is important to realise that the forward rectified voltage varies directly with the forward r.f. power in the line. With this thought in mind, consider a linear r.f. amplifier.

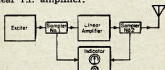


Fig. 1—Block diagram of the linearity metering setup. Two identical r.f. sampling devices are used with their outputs fed into a comparison circuit. The adjusting potentiometer is calibrated in db, and indicates the gain of the linear.

Within the limits of linearity, the ratio of output power to input power is constant. If identical r.f. sampling devices are inserted in the input and output coaxial lines of such an amplifier, as shown in Fig. 1, the ratio of the forward rectified voltages from the two sampling units will be constant within the limits of linearity of the amplifier. By using a zero-centre scale voltmeter and a comparison circuit with a

• The author presents a unique but simple device for use with a linear r.f. amplifier that indicates relative input and output power, input and output s.w.r., and amplifier linearity deviation.

potentiometer for equalising the ratio of the forward rectified voltages from the sampling devices, a visual indication of the linearity deviation can be obtained. The indication is derived from true dynamic conditions. Since the adjustment of the equalising potentiometer is a function of the power gain of the amplifier, this potentiometer can be calibrated in terms of db. gain or other acceptable units.

Data for the calibration of the potentiometer in db. is given in Table 1 and the derivation of Table 1 is explained at the end of this article. This potentiometer can be calibrated with a reliable ohmmeter.

Gain, db.	X, Ohms	Y, Ohms
0	10,000	0
2	8,854	1,146
4	7,738	2,262
6	6,677	3,323
8	5,695	4,305
10	4,805	5,195
12	4,015	5,985
14	3,326	6,674
16	2,736	7,264
18	2,236	7,764
20	1,818	8,182

Table 1—Calibration data for the Linearity Balance potentiometer. Areas X and Y of the potentiometer are identified in Fig. 2.

As explained, two r.f. sampling devices and a zero-centre meter are required to indicate linearity deviation. By incorporating a switch, an additional potentiometer and a few resistors, the meter and sampling devices can be connected to indicate the functions listed below:—

- Amplifier Input—Relative Forward Power.
- Amplifier Input—Reflected Power—S.W.R.
- Linearity Deviation.
- Amplifier Output—Reflected Power—S.W.R.
- Amplifier Output—Relative Forward Power.

CONSTRUCTION

The circuit of the complete unit is shown in Fig. 2. The operation of the two s.w.r. bridges is conventional and is described in the handbooks. The instrument housing should be large enough to contain the two potentiometers, the five-section switch and the four 10K, 1 watt, resistors. The four phono jack type connectors are located on the rear of the cabinet. Wiring is not particularly critical.

Construction data for the line samplers is shown in Fig. 3. The units are made from 1" aluminium angle stock. The main conductor, 3/16" o.d. copper tubing, is connected to the two hot lugs of the coax connectors (in this case type C) and if the measurements are followed exactly, they will be 3-7/8", centre to centre.

The 1" thick polystyrene blocks support the two 12 gauge copper wire sampling lines.

Fig. 4 shows a suggested panel arrangement of the unit and a tabulation of meter readings against the standing wave ratio. A photograph of the unit is not shown since it is an integral part of the author's 1kw. linear amplifier and would show very little if any detail.

OPERATION

Application of this unit is explained for each function.

Input S.W.R.—Throw the selector switch to the **input forward** position. Apply carrier excitation to the amplifier and adjust the s.w.r. sensitivity control for full scale deflection of the meter. Throw selector switch to **input reflected** position and adjust grid circuit tuning of the r.f. amplifier for minimum meter reading.

Output S.W.R.—Throw the selector switch to **output forward** position and, with carrier, adjust s.w.r. sensitivity control for full scale deflection of meter. Throw selector switch to **output reflected** position and read standing wave ratio of amplifier load.

* Reprinted from "CQ," October, 1962.

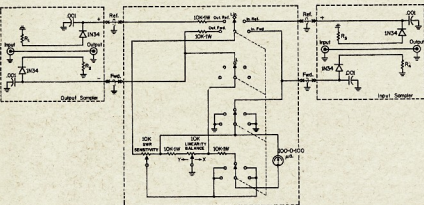


Fig. 2—Circuit of the S.W.R. Bridge/Linearity Indicator. The value of resistors R1 to R4 is determined by the coax cable impedance. For 52 ohms 175 ohms 1 watt carbon resistors are used. For 72 ohm coax, the value should be approximately 240 ohms.


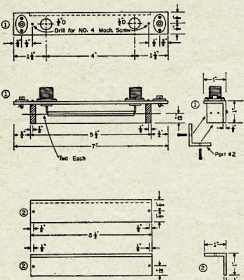


Fig. 3.—Construction data for the two identical sampler units to be inserted before and after the linear amplifier. The stock is $\frac{1}{2}$ x 1 inch aluminium angle.

Linearity.—With full carrier inserted, and the amplifier operating under full load, throw selector switch to **linearity** position and adjust the **linearity balance** potentiometer for zero meter reading. Remove full carrier excitation and place amplifier in normal operating condition. If the amplifier is linear, the indicating meter will not deviate from zero during amplifier operation. When the **linearity balance** potentiometer is adjusted as described, the potentiometer setting indicates the db. gain of the amplifier.

As indicated previously, in linear operation there should be no shift in the meter indication at all. In the absence of linear operation the deviation shown by the meter would vary with the amount of excitation. The shift could be caused by improper grid bias, parasitics, improper plate and/or screen voltage, improper amplifier loading or by any combination of these conditions. The operator should be concerned about any meter deflection of more than five microamperes and

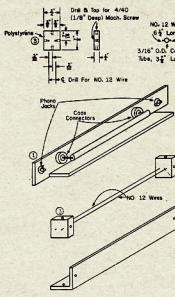

From the above then:

$$\begin{aligned} E_1 &= I_1 X \\ E_2 &= I_2 (R - X) \\ E_3 &= E_2 - E_1 \text{ (Note polarity)} \\ E_3 &= E_2 - I_1 X = I_2 (R - X) \\ \frac{I_1}{I_2} &= \frac{R - X}{X} \end{aligned}$$

The ratio of voltages E_1 and E_2 can be expressed:

$$\text{db.} = 20 \text{ Log } \left(\frac{E_2}{E_1} \right)$$


Similarly, the ratio of currents I_1 and I_2 can be expressed:

$$\text{db.} = 20 \text{ Log } \left(\frac{I_1}{I_2} \right)$$

$$\text{Substituting: db.} = 20 \text{ Log } \left(\frac{R - X}{X} \right)$$

Note that when $db. = 0$, $R - X = X$. Also, when the pot. is adjusted so that $E_s = 0$, the pot. setting $[(R - X) \div X]$ can be calibrated in db.

Practical Application

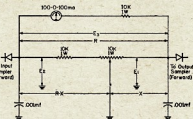

From the theoretical analysis it may be seen that, when $E_1 = E_2$, $E_3 = 0$ and

$$\text{db.} = 20 \text{ Log } \left(\frac{R - X}{X} \right)$$

the following chart (Table 2) may be derived as was given in abbreviated form in Table 1. ●

ADDENDUM

While it is not necessary for the construction of the unit, some readers may desire an understanding of the computations involved in determining the resistance points necessary to calibrate the linearity balance potentiometer in terms of db. of amplifier gain. The explanation is divided into two parts; first a purely theoretical analysis and secondly, the practical application.

Theoretical Analysis



R = Total potentiometer resistance
in ohms.

X = Resistance of portion of pot.
to right of arm, in ohms.

-X = Resistance of portion of pot.
to left of arm, in ohms.

E_1 = Voltage across portion of pot.
to right of arm.

E_2 = Voltage across portion of pot.
to left of arm.

E_x = Total voltage across pot.
 I = Current through X portion of

I_1 = Current through A portion of pot.
 I_2 = Current through B & Y non

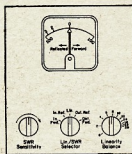


Fig. 4.—Suggested panel arrangement. The s.w.r. calibration marks shown correspond as follows: An s.w.r. of 1:1 equals 0 μ A., 2:1 equals 63.5 μ A., 3:1 equals 86.6 μ A. on the meter scale.

Gain db.	R - X Ohms	X Ohms	R - X X	Log ($\frac{R-X}{X}$)
0	10,000	10,000	1.0000	0.0000
1	11,146	8,854	1.2588	0.1000
2	12,922	7,738	1.5848	0.2000
3	13,323	6,677	1.9952	0.3000
4	14,305	5,695	2.5117	0.4000
5	15,195	4,805	3.1621	0.5000
6	15,985	4,015	3.9809	0.6000
7	16,674	3,326	5.0122	0.7000
8	17,264	2,736	6.3100	0.8000
9	17,764	2,236	7.9433	0.9000
10	18,182	1,818	10.0000	1.0000

Table 2.

W.I.A. 50 Mc. W.A.S.			
Call	Cer. Add. No. Cntr.	Call	Cer. Add. No. Cntr.
VK4HD	27 8	VKS5BQ	23 3
VK4ZAZ	26 7	VK7LZL	24 3
VK4ZBE	20 6	VKS2HF	25 3
VK5WJ	13 4	VK9AU	32 3
VKS2FM	22 4	VKS2GZ	28 2
VK5IM	30 4	VKS2ZT	31 2
VK4PU	26 7	VKS2ZU	31 2
VK4HR	4 3	VKS2MK	38 2
VK3PG	5 3	VK7ZAQ	34 1
VK3ABC	8 3	VKS2BR	37 1
VK3W	9 3	VKS5AX	36 -
VK5GG	19 3		

HIGH FREQUENCY CRYSTAL FILTERS

ARIE BLES, VK2AVA

CRYSTAL filters on frequencies between 5 and 9 Mc. are now being used in many commercial Amateur transmitters and transceivers. The McCoy crystal filter on 9 Mc. can be bought as a separate unit and provides an excellent basis for a simple s.s.b. rig, but the \$32.50 U.S.A. price would be a lot higher before it is in your shack.

Some Amateurs have tried filters with FT243 surplus crystals with limited success, regardless of the claims made in articles in "QST" of January 1959, May 1960, and October 1960. The filter bandpass curves published in these articles are difficult to duplicate, at least I have never had success myself.

The advantages of a high frequency filter are obvious. One can save at least one stage or sometimes two stages of frequency conversion. Consequently there are less oscillators producing unwanted spurious frequencies and less risk of frequency conversion and mixing distortion and unwanted by-products. In particular for the v.h.f. bands, a s.s.b. transmitter starting with a 450 Kc. sideband generator will become quite involved.

My earlier experiments were made with a limited supply of 5,000 Kc. crystals. A lot of work is required to not only check their zero and anti-resonance frequencies, but some have to be changed in frequency to obtain matched pairs and invariably one will overshoot the desired frequency and loose crystals. Recently I have had the luck to play with several hundreds of crystals of the same frequencies and that offered a much better chance to arrive at something.

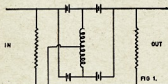


FIG. 1.

As explained in the "QST" articles referred to, the recommended circuit is not a standard half-lattice set-up but a hybrid circuit, using four crystals, two pairs of two crystals closely matched in frequency and between 1,500 and 2,000 cycles in frequency apart. This is being done to make the second higher frequency pair of crystals to fall on the so-called pole-frequency of the first lower frequency pair of crystals.

All crystals, when used as filters, will demonstrate two distinct resonance points, one, the lower frequency one, where the r.f. resistance of the crystal is lowest, its zero resonance point, and a second frequency, higher than the zero resonance point, where the resistance is largest, its parallel or pole frequency point. If the zero frequen-

cies of the second pair match the pole frequencies of the first pair, it is supposed to provide a flat bandpass curve.

The centre tapped tuned circuit (as in Fig. 1) between the four crystals has always given me trouble. Some sources say tight coupling is a necessity, so use a bi-flar wound coil. Others say, no, tune the circuit to resonance and use a standard good quality coil and that will do the trick. Others again say a high quality toroid coil core is a necessity, a.s.o. But all have had trouble to flatten the peaks and valleys in the bandpass. They use rather low resistors at both ends of the filter to swamp the circuit and are obviously trying to smooth out the bandpass curve.

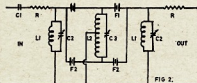


FIG. 2.

- C1—0.002 μ F.
- C2—50 pF.
- C3—30 pF, Philips trimmer, about half capacity.
- L1—Iron slug tuned coil, approx. resonating on 5.5 Mc.
- L2—17 turns bi-flar wound litz wire on Command Set iron core (34 turns).
- F2—F1 plus 1,500 to 2,000 cycles.
- R—2,000 ohms.

I have never been able to lay my hands on a genuine toroid coil core, so at last tried my luck with a powdered iron core out of the final tank coil of a Command transmitter. It is about $\frac{3}{4}$ " in diameter and $\frac{1}{4}$ " long, and the small hole in the centre can be enlarged with an ordinary drill. Seventeen turns of bi-flar wound litz wire and a Philips pot trimmer gave better results than anything I had tried before, but still that blasted trouble to smoothen the humps in the bandpass curve.


Well, to cut a long story short, instead of swamping the filter with resistors I have loaded it with tuned circuits and inserted series resistance in the input and output of the filter. In this manner I could immediately improve the bandpass curve, get an almost perfect flat bandpass with nice steep sides, obtain a good shape factor, and flatten out slight irregularities in the curve with small adjustments of the three tuned circuits in the filter. The procedure is to tune for maximum response on the frequency half way between those of the crystals and next make slight adjustments, one way or the other, of the tuned circuits, no more.

Do not ask me why this arrangement works in preference over and better than what others have used. The main thing is it works well without much trouble of alignment. The series

resistances involve some loss of signal but probably much less than parallel resistance swamping; the impedance of this circuit is of course much higher. I shall not apply for a patent on the circuit—yet.

Considering the work involved to select suitable crystals and the fairly large number required to obtain useable pairs that will match, I am going to offer help again to those who want it, like in the case of the 60 odd sets of 400 Kc. crystals that have found their destination.

I have been allowed access to large numbers of crystals, FT243 surplus types, procured by the N.S.W. section of the W.I.A., and am already checking, matching and testing them in this circuit of mine. A set of four crystals, matched in frequency and response, plus two carrier oscillator crystals, selected and carried to fall on the 20 db. down points of the bandpass curve of the particular set of four crystals, on 5436 Kc., or after exhausting the supply of those crystals, elsewhere between 5 and 6 Mc., will be available to genuinely interested Amateurs on direct application to me for three guineas, post paid.

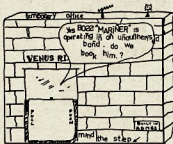

NAT. FIELD DAY 1963

The National Field Day Contest will be held on Saturday, 9th February, and Sunday, 10th February. The rules appeared on page 17 of the last issue.

ADDITIONAL RULE 6A

Entrants to Section C for Multiple Operator Stations can set up separate transmitters to work on different bands at the same time. All such units of a Multiple Operator Station must be located within an area that can be encompassed by a circle not greater than half a mile diameter.

For each transmitter of a Multiple Operator Station a separate log shall be kept with serial numbers starting from 001 and increasing by one for each successive contact. All logs of a Multiple Operator Station shall be submitted by the Operator under whose Call Sign the transmitters are working. No two transmitters of a Multiple Operator Station are permitted to operate on the same band at any time.

1A recommended type is the Mullard FX1299.
—Editor.



WARBURTON FRANKI

for your Radio and T.V. Accessories

BIGGER RANGE BETTER VALUES

NEW TRIPLE PLAY RECORDING TAPE

Agfa: 3" 450' 24/8 plus tax 12½%
 4" 900' 39/- plus tax 12½%
 5" 1800' 64/4 plus tax 12½%
 5½" 2400' 76/8 plus tax 12½%
 7" 3600' 118/4 plus tax 12½%

MAGNAVOX QUALITY SPEAKERS AT A SENSIBLE PRICE

For Columns

... use the 6WR, 15 ohm Voice Coil,
 6½" max. diameter, 30 to 15,000 c.p.s.,
 6 watts peak.

84/9 plus tax 25%

For Stereo

... use a pair of 8WR's, 2.7 or 15 ohm
 Voice Coil, 8-3/16" max. diameter, 30
 to 15,000 c.p.s., 7 watts peak.

91/3 plus tax 25%

For High Class Mono or Stereo

... the 12WR is supreme. 2.7 or 15
 ohm Voice Coil, 12½" max. diameter,
 30 to 15,000 c.p.s., 10 watts peak.

97/9 plus tax 25%

The above Speakers all have a gap flux
 density of 11,500 gauss and a bass
 resonance of 45 c.p.s.

Write or call for enclosure data; also
 information on the complete Magnavox
 range.

EXTRA SPECIALS:

Power Transformers, A. & R. Type 1917:

280/0/280 V. at 50 mA.
 6.3 V. at 1.8 A.
 6.3 V. at 600 mA.
 16 V. at 450 mA.

20/- plus tax 25%

Power Transformers, A. & R. Type 1916:

325/0/325 V. at 70 mA.
 6.3 V. at 2.25 A.

24/- plus tax 25%

Step-Down Transformers, Three Only:

240 V. to 32 V. at 500 Watts.
 Fully cased, 2-pin outlet.

To Clear: £13 plus tax 12½%

Step-Down Transformers, Three Only:

240 V. to 110 V. at 500 Watts.
 Open type, conduit entry and exit.

£8/10/0 plus tax 12½%

Power Diodes:

700 mA. at 500 P.I.V.

9/6 ea. plus tax 25%

Panel Meters:

4" square case, 0-1 mA.

67/6 ea. sales tax exempt

Voltage Doubler Transformers:

Small size, suitable Tuners, etc.

S.E.C. 0/136 V. at 25 mA.

6.3 V. at 1.25 A.

15/- plus tax 25%

IMPORTED KNOBS

1½" diam. 5/8" deep. Standard 1"
 bore. White rim with black top.
 Golden arrow moulded into top.

No. 2124. 2/2 ea. plus tax 25%

IMPORTED PLUGS AND SOCKETS

7-pin miniature, line-to-line type.

3/9 plus tax 25%

2-pin miniature, line-to-panel type.

2/8 plus tax 25%

IMPORTED BANANA TYPE PLUGS

Suprax.

Fits standard size banana sockets.

Straight type 7/9 doz. plus tax 25%

Angle type 9/3 doz. plus tax 25%

Also available with spade end

..... 7/9 doz. plus tax 25%

Suprax Plugs are convenient to use
 as the lead is simply held in place by
 spring tension. It is removed by press-
 ing a button.

IMPORTED MINIATURE ELECTROLYTIC CAPACITORS

Nichicon

Available in the following ranges:—

6 Volt Working: 2 and 5 µF. 2/-
 10 µF. 2/1
 25 and 50 µF. 2/2
 100 µF. 2/4

12 Volt Working: 2 and 5 µF. 2/-
 10 µF. 2/1
 25 µF. 2/4
 50 µF. 2/5
 100 µF. 2/6

25 Volt Working: 2, 5 and 10 µF. 2/4
 25 µF. 2/5
 50 µF. 3/2
 100 µF. 3/9

50 Volt Working: 2 and 5 µF. 2/4
 10 µF. 2/5
 50 µF. 3/3

All above Capacitors plus tax 25%.

- OPEN SAT. MORNING
- TRADE ALSO SUPPLIED

Please include postage or
 freight with all orders.

Amateur Radio, February, 1963



WARBURTON FRANKI

359 LONSDALE ST., MELBOURNE — MU 8351



MORE ABOUT FT241 SURPLUS CRYSTALS

ARIE BLES, VK2AVA

MILLIONS of these crystals must have been made during the last war as they are still plentiful—unfortunately not in this country. They were made for the SCR508 f.m. transceivers that operated from tanks on frequencies between 20.0 and 38.9 Mc. at 0.1 Mc. intervals. The crystals are marked with these frequencies but their basic frequencies are actually between 370 and 540 Kc. In the tank sets where they were used, the modulation was applied to the crystal oscillator and the resultant phase modulated signal was multiplied 54 or 72 times, depending upon the use of the crystal and the series in which it belongs.

There are two groups of crystals (see Tables next page):—

- (a) Those in **black holders**, marked 20.0 to 27.9 Mc. with channel numbers 0 to 79; crystal frequencies 370.370 to 516.667 Kc. (never exact) in steps of 1,851 cycles apart.
- (b) Those in **brown holders**, marked 27.0 to 38.9 Mc. with channel numbers 270 to 389; crystal frequencies 375.000 to 540.277 Kc. (may be as much as 250 to 300 cycles off) in steps of 1,389 cycles apart.

Because those crystals had to be used in tanks, they are ruggedly built, but still they may be defective now. The crystals are only about $\frac{3}{8}$ " to $\frac{1}{2}$ " square, as thin as a normal 7 Mc. crystal, they vibrate transversally, and their size determines their frequency.

They were originally silver or gold plated, small thin wires soldered in the centre of the crystal-electrodes faces, and these small $\frac{1}{8}$ " wires soldered on to springy sort of suspension wires that are attached to pins spaced $\frac{1}{8}$ " apart.

* 33 Plateau Road, Springwood, N.S.W.

● The author's recent contribution to Bud Pounsett's s.s.b. column has raised the interest in those very useful FT241A crystals and here is a set of details regarding them.

I cannot express it in g's acceleration, but know from experience that a good crystal will easily survive a drop on to a concrete floor from a height of four feet (not recommended as a test!).

On the average these crystals are good and vigorous oscillators, but there are bad ones amongst them—discounting the ones where the little wires on the crystal-electrodes faces have come loose (this is mainly due to corrosion of the electrodes and consequent loss of crystal activity). Remedies, however, both for loose contact wires and corroded electrodes are possible.

When one of the little wires has come loose, do not throw away your crystal. If you check the small dot of solder on the crystal electrode, using a magnifying glass or loupe, you will frequently see a little hole in it where the wire has been in before it came loose. Carefully bring the wire back in position, bend one of the spring-wires a little to create some pressure to the crystal and hold the contact wire in place and your crystal very likely will be OK again.

Loss of activity due to corroded electrodes is very common with crystals that were improperly stored, as many must have been. The remedy is to re-silverplate the crystal. There apparently is always enough material left to conduct for plating and you can obtain a crystal that will be active on a lower frequency like a new crystal. For the

plating, one could also use a copper-sulphate solution, but it is inferior to silverplating with a silvernitrate solution. Many formulae exist for silverplating, none work as well as a special cyanate professional plating solution that is rather poisonous and must be handled with care.

The frequencies of the crystals can be shifted up and down with extreme care sometimes, but it is possible. To lower the frequency up to over 2,000 cycles, one can weight the electrodes either by silverplating or, for a limited shift, by simply rubbing some carbon on to them with a soft pencil. For that operation, hold the crystal steady between two fingers and watch where the pencil tip goes. If you touch the contact wires too often, they may come loose. Silverplating should be done with not more than 1 mA. plating current. A $1\frac{1}{2}$ volt cell and a 1,000 ohm resistor in series are safe. The crystal should be on the negative side of the battery.

To raise the frequency of the crystal is more difficult. Never try to take off some of the material of the electrodes by reversing the plating procedure. There is never much thickness in the electrodes and you risk that all of a sudden you have a nice clean transparent crystal left! The only way to raise the frequency is by edge-grinding the crystal. Some sources have recommended to unsolder the contact wires and then to hold the crystal in your fingers while edge-grinding. Personally, I prefer to use a pair of small tweezers to hold the sides of the crystal with the bottom part of the crystal-holder still attached and lying flat on the table and gently move a thin grinding stone along one edge of the crystal. I have managed to raise the frequency that way 20 and more Kc.,

CRYSTALS for Lattice Filters and S.S.B. Equipment

FT-241 Crystals in MATCHED PAIRS ± 5 CYCLES are available in following frequencies:

444.444 Kc.	451.852 Kc.	459.259 Kc.	464.815 Kc.	Price per MATCHED PAIR
446.296 Kc.	453.704 Kc.	461.111 Kc.	466.607 Kc.	£3/12/6
448.148 Kc.	457.407 Kc.	462.963 Kc.	468.519 Kc.	Includes sales tax and one
450.000 Kc.			470.370 Kc.	dual crystal socket.

455.000 Kc. Crystals, £2/0/0 each, includes sales tax and crystal socket.

HC6/U 100 Kc. Marker Crystals, £4/16/0 each, includes sales tax and crystal socket.

FX-1 Type Crystals, 0.001% accuracy: 1,000 Kc., £5/15/6; 3,500 Kc., £4/6/6

FA-5 Type Crystals, 0.01% accuracy: 1,500 Kc., £4/17/6; 7,000 Kc., £5/8/0
14,000 Kc., £6/8/3; 21,000 Kc., £5/8/0

Prices of Crystals on any frequency upon request.

Prices include sales tax and ceramic socket.

All goods despatched by Certified Mail. Be sure to include your full address and cheque or money order with your order.

PHONE OR MAIL ORDERS ONLY
NO CALLERS PLEASE
XJ 6181, XJ 2353

TRANSTRONIC PRODUCTS
123 BALGOWLAH ROAD, FAIRLIGHT, N.S.W.

but it takes time and patience and one wrong movement and the crystal may be cracked or the contact wires damaged.

For many filter applications the crystals should either be paired in frequency or raised or lowered for oscillator use. For those that smoke too much to have steady hands and fingers, or anyway feel reluctant to touch their crystals, I offer my help to adjust and match the crystals they may have. I could also at the same time set up a sort of crystal exchange bank. A dozen possessors of odd channels of crystals together may have enough to form useable pairs with little adjustments. But not to expect and swap odd frequency ones for the elusive 455 Kc. rocks. Also, after quickly distributing sets of four paired crystals to what I hope some 50 future s.s.b. operators, my stock of crystals is long exhausted and I am going to get a fresh supply somehow from overseas again at reasonable prices. When available it will be announced in "A.R."

DURALUMIN, ALUMINIUM ALLOY TUBING

IDEAL FOR BEAM AERIALS AND T.V.

★ LIGHT ★ STRONG ★ NON-CORROSIVE

STOCKS NOW AVAILABLE FOR IMMEDIATE DELIVERY

ALL DIAMETERS— $\frac{1}{4}$ " TO 3"

Price List on Request

STOCKISTS OF SHEETS—ALL SIZES AND GAUGES

GUNNERSSEN ALLEN METALS PTY. LTD.

SALMON STREET,
PORT MELBOURNE, VIC.

Phone: 64-3351 (10 lines)
Telegrams: "Metals," Melb.



HANSON ROAD,
WINGFIELD, S.A.

Phone: 45-6021 (4 lines)
Telegrams: "Metals," Adela.

FUNDAMENTAL FREQUENCIES OF FT241 CRYSTALS

Chan. nel No.	Fund. Fre- quency	Marked Fre- quency	Chan. nel No.	Fund. Fre- quency	Marked Fre- quency	Chan. nel No.	Fund. Fre- quency	Marked Fre- quency	Chan. nel No.	Fund. Fre- quency	Marked Fre- quency	Chan. nel No.	Fund. Fre- quency	Marked Fre- quency
0	370.370	20.0	16	400.000	21.6	32	429.630	23.2	48	459.259	24.8	64	488.889	26.4
1	372.222	20.1	17	401.852	21.7	33	431.481	23.3	49	461.111	24.9	65	490.741	26.5
2	374.074	20.2	18	403.704	21.8	34	433.333	23.4	50	462.963	25.0	66	492.593	26.6
3	375.926	20.3	19	405.556	21.9	35	435.185	23.5	51	464.815	25.1	67	494.444	26.7
4	377.778	20.4	20	407.407	22.0	36	437.037	23.6	52	466.667	25.2	68	496.296	26.8
5	379.630	20.5	21	409.259	22.1	37	438.889	23.7	53	468.519	25.3	69	498.148	26.9
6	381.481	20.6	22	411.111	22.2	38	440.741	23.8	54	470.370	25.4	70	500.000	27.0
7	383.333	20.7	23	412.963	22.3	39	442.593	23.9	55	472.222	25.5	71	501.852	27.1
8	385.185	20.8	24	414.815	22.4	40	444.444	24.0	56	474.074	25.6	72	503.704	27.2
9	387.037	20.9	25	416.667	22.5	41	446.296	24.1	57	475.926	25.7	73	505.556	27.3
10	388.889	21.0	26	418.519	22.6	42	448.148	24.2	58	477.778	25.8	74	507.407	27.4
11	390.741	21.1	27	420.370	22.7	43	450.000	24.3	59	479.630	25.9	75	509.259	27.5
12	392.593	21.2	28	422.222	22.8	44	451.852	24.4	60	481.481	26.0	76	511.111	27.6
13	394.444	21.3	29	424.074	22.9	45	453.704	24.5	61	483.333	26.1	77	512.963	27.7
14	396.296	21.4	30	425.926	23.0	46	455.556	24.6	62	485.185	26.2	78	514.815	27.8
15	398.148	21.5	31	427.778	23.1	47	457.407	24.7	63	487.037	26.3	79	516.667	27.9

Chan. nel No.	Fund. Fre- quency	Marked Fre- quency	Chan. nel No.	Fund. Fre- quency	Marked Fre- quency	Chan. nel No.	Fund. Fre- quency	Marked Fre- quency	Chan. nel No.	Fund. Fre- quency	Marked Fre- quency	Chan. nel No.	Fund. Fre- quency	Marked Fre- quency
270	375.000	27.0	294	408.333	29.4	318	441.666	31.8	342	475.000	34.2	366	508.333	36.6
271	376.388	27.1	295	409.722	29.5	319	443.055	31.9	343	476.388	34.3	367	509.722	36.7
272	377.777	27.2	296	411.111	29.6	320	444.444	32.0	344	477.777	34.4	368	511.111	36.8
273	379.166	27.3	297	412.500	29.7	321	445.833	32.1	345	479.166	34.5	369	512.500	36.9
274	380.555	27.4	298	413.888	29.8	322	447.222	32.2	346	480.555	34.6	370	513.888	37.0
275	381.944	27.5	299	415.277	29.9	323	448.611	32.3	347	481.944	34.7	371	515.277	37.1
276	383.333	27.6	300	416.666	30.0	324	450.000	32.4	348	483.333	34.8	372	516.666	37.2
277	384.722	27.7	301	418.055	30.1	325	451.388	32.5	349	484.722	34.9	373	518.055	37.3
278	386.111	27.8	302	419.444	30.2	326	452.777	32.6	350	486.111	35.0	374	519.444	37.4
279	387.500	27.9	303	420.833	30.3	327	454.166	32.7	351	487.500	35.1	375	520.833	37.5
280	388.888	28.0	304	422.222	30.4	328	455.555	32.8	352	488.888	35.2	376	522.222	37.6
281	390.277	28.1	305	423.611	30.5	329	456.944	32.9	353	490.277	35.3	377	523.611	37.7
282	391.666	28.2	306	425.000	30.6	330	458.333	33.0	354	491.666	35.4	378	525.000	37.8
283	393.055	28.3	307	426.388	30.7	331	459.722	33.1	355	493.055	35.5	379	526.388	37.9
284	394.444	28.4	308	427.777	30.8	332	461.111	33.2	356	494.444	35.6	380	527.777	38.0
285	395.833	28.5	309	429.166	30.9	333	462.500	33.3	357	495.833	35.7	381	529.166	38.1
286	397.222	28.6	310	430.555	31.0	334	463.888	33.4	358	497.222	35.8	382	530.555	38.2
287	398.611	28.7	311	431.944	31.1	335	465.277	33.5	359	498.611	35.9	383	531.944	38.3
288	400.000	28.8	312	433.333	31.2	336	466.666	33.6	360	500.000	36.0	384	533.333	38.4
289	401.388	28.9	313	434.722	31.3	337	468.055	33.7	361	501.388	36.1	385	534.722	38.5
290	402.777	29.0	314	436.111	31.4	338	469.444	33.8	362	502.777	36.2	386	536.111	38.6
291	404.166	29.1	315	437.500	31.5	339	470.833	33.9	363	504.166	36.3	387	537.500	38.7
292	405.555	29.2	316	438.888	31.6	340	472.222	34.0	364	505.555	36.4	388	538.888	38.8
293	406.944	29.3	317	440.277	31.7	341	473.611	34.1	365	506.944	36.5	389	540.277	38.9

SIDEBAND TOPICS—BUD POUNSETT,* VK2AQJ

How do you like the new presentation of this department? The general opinion on the air seems to be very much in favour. The success of Sideband Topics depends on YOU.

Do you have anything that is of interest to your fellow sidebanders? If so, please send it along to me and also note my new address. The information that I require is items about single sideband or an allied subject of a technical nature. What about, it OM, will you do your bit?

288 Mc. S.S.B.

Lance Harding (VK3AHL), of Melbourne, no longer has the distinction of being the world's only 288 Mc. s.s.b. operator. On December 9, Lance was joined by Jack VK3ZLC. On that

original circuit, and to warn you of the traps, here they are.

The 6CL6 driver tube does not have any bias on it. This is easily remedied by placing a 100 ohm resistor bypassed by a 0.01 μ F. disc ceramic capacitor between pin 1 and ground. The circuit diagram has pins 4 and 5 as heater connections for the 6146 and these should be pins 2 and 7. The tuned circuit between the transmitter mixer, a 12AT7 and the 6CL6, is a pi network and was replaced by a normal parallel tuned circuit with capacitive coupling. This was found to be easier to adjust.

The crystal in the original was for operation between 7.2 and 7.3 Mc., this being the American 40 metre phone band. For use in Australia the crystal frequency required is 5,700 Kc., which is readily available from disposal

The circuit in Fig. 2 was used to speed up the operation. With the vox relay open, there is no current flowing in the resistor R and the relay coil, so the voltage at the 100 μ F. capacitor is 12 volts. Closing the vox relay contacts discharges the capacitor through the antenna relay coil, pulling the relay in very rapidly. The resistor R now drops the voltage to the correct hold-in voltage for the antenna relay. The value of R can be determined by the application of ohm's law. Do not forget to also take the power dissipated in the resistor into account.

I do not know how fast in milliseconds this system is, but it is rapid enough to cause no noticeable clipping of the first syllable.

OPERATING PROCEDURE

Just two comments this month, one on breaking-in and another about that "ah". Last month I mentioned a suggested form of joining a net. When you do break-in by giving your call sign at an appropriate moment, do so in much the same way as knocking on a door, then wait until you are invited in. When you are invited in, acknowledge all the members in the room—I should say, net—do not just address your remarks to one station and ignore the rest; this is ill-mannered.

Also when a station is calling CQ, try using break-in procedure as soon as you have his call sign. This saves lots of time and breath but does not seem to be in use today so much as it has in the past. You will be surprised how effective this can be used on DX station. You may be able to beat all the rest who are lined up on the frequency waiting for him to finish his CQ.

How often have you run across the operator who cannot stand to have his vox drop out? This is the one who uses "ahs" and "ers" for commas, full stops and even several of either between paragraphs. How he ever manages to take a breath is beyond me. It is rather difficult to tell him of this exasperating habit—he will not mind if you tell him his signal is broad or distorted if it is, but this "ah, ah, ah" habit! Extreme tact would be required. However there is a way, although not available to everyone. If you have tape replay facilities, you might ask him if he would like to hear his own transmission. One usually listens rather critically to one's own voice, so he is sure to notice. Another method available to every one of us is to listen carefully to the way we speak ourselves. Next time you are having a contact, examine your own speech for these most unnecessary sounds.

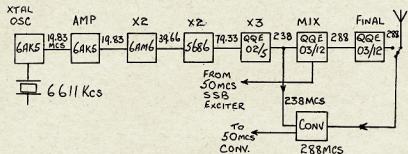


Fig. 1—VK3ZLC 288 Mc. equipment.

Sunday, Lance and Jack made, we believe, the first two-way s.s.b. contact on the 288 Mc. band. These two pioneers have been working together on this project and naturally some of their equipment is identical. Their converters are the same as that outlined in "A.R."

The antennae used are 13 element long yagi beams. There is some difference in the transmitters. Both use 50 Mc. s.s.b. injection, but the VK3ZLC transmitter mixes in a 6QE03/13 balanced mixer driving a 6QE03/12 linear amplifier to about two to three watts peak output. Congratulations to two worthy gentlemen who are certainly doing their share in upholding one of the best of Amateur traditions.

KWM-1 AND 40

There are a few KWM-1 transceivers in use around Australia and no doubt there will be a few more as time goes by, even though they are no longer in production. The one disadvantage of this very fine equipment is that 40 and 80 metres is not covered, only operation on 20, 15 and 10 being possible.

Recently (August 1962) "CQ" published an article on a converter, or to use the modern term, a transverter, to permit operation on 7 Mc. This takes the form of a receiver front end and an s.s.b. transmitter rear end. It does not require any modification to the M-1. To get to the point in mentioning this "CQ" article, John VK2BM found that an error or two has crept into the

sources, having been used in at least two different equipments, a walkie-talkie and a glide path receiver.

For those of you who wish to consult the original article, it is called "Adaptor for the KWM-1 to 40 Metres" by Tal Lawrence, 25GVZ and can be found in "CQ" magazine, August 1962, page 32.

RELAY ACCELERATION

You may have the same problem that I had some months ago. I required my vox relay to operate a coaxial antenna relay having auxiliary contacts. The auxiliary contacts are used to control the transmitter and receiver so that antenna change-over and transmitter switch-on are sequenced by the relay. The problem was to shorten the time interval between the first sound into the microphone and the antenna relay operating. The vox relay, a 5,000 ohm squelch relay, from an SCR522 receiver, operates very quickly, but the 6 volt d.c. antenna relay was rather sluggish.

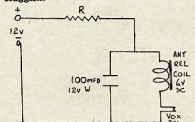


Fig. 2—Faster Relay Operation.

CHANGE OF ADDRESS

W.I.A. members are requested to promptly notify any change of address to their Divisional Secretary, not direct to "Amateur Radio."

* 7 Thorpe Ave., Queenbeyan, 45, N.S.W.

VHF NOTES

(Continued from Page 15)

59 Mc.: A number of breakthroughs have been observed in VK6. All States with the exception of VK8 have been worked consistently this season. Brian 6VV at Geraldton has been conducting regular sdxs with Bob 6BE over the nth/ath. path and has also worked this path on 144 Mc.

Kevin 6ZCB and his XYL Pam went on a DX-pedition to Esperance on the south coast and worked numerous stations in the east.

A number of the Group went to Rottnest Is., 13 miles off the coast, for a week over Xmas. They had both 50 and 144 Mc. gear and among those with call signs were 6DI, 6ZBT, 6ZCP, 6ZDW and, I think, 6ZDX. They worked local stations on both bands and also quite a bit of DX. David 6DI received c.w. sigs from Don 6HK by light beam. Don was using a 50w. spotlight modulated by the power switch. If nothing else, it proves Wembley and Rottnest are line of sight for v.h.f. transmissions.

144 Mc.: There are reports of more activity on this band. Viv 6ZCM has a 523 operating and has been using it for quite a bit of cross band operating. Neil 6ZDK has been testing a new tx he has almost completed, using a Gelson front-end and an 832 final. It has a built-in modulator. The filaments have been wired to operate off either 6 or 12 volts, so it should be a very versatile unit when completed and operating.

288 Mc.: After conducting test transmissions for some time, the t.v. fraternity had a live night recently. The broadcast, which lasted over two hours, included demonstrations of camera work, building a converter for Amateur t.v. reception, a 144 Mc. link enabled questions on the demonstration to be answered. Jack 6BU had a number of the V.h.f. Group interested in Amateur t.v. at his QTH to view the demonstration.

1. would like to pass on the V.A. V.h.f. Group's best wishes for '63 to all our counterparts in other States. TX, 6ZDM.

PAPUA

6 mx produced some good DX openings during Dec. VK4s were worked on 2nd, and on 16th VK2, 3, and 4 were worked. 64h, VK4s worked and 72A1 heard. VK4s again on 27th. A few weak VK4s and 3s heard on 29th. A rather weak opening occurred on 30th when numerous VK2, 3, 4, and 7 were heard, however only 6ZAZ was worked. A few very weak signals heard on 31st, whilst New Year's Day produced excellent DX, signals being heard and worked for over 12 hours. Call areas worked were VK2, 3, 4, 5, and 7. TE scatter signals on 49.9 Mc. were heard on the 17th.

As 6ZBV has been in Rabaul, no local 2 mx working took place during the month and tests with VK4 produced no results.

T.v. reception was quite good with signals being seen from TNQ7, ABQ2, ABN2, ABV2, ABS2, and ABT2. TX, 9AU.

BROADCASTING

Modern and well equipped Commercial Broadcasting Station invites applications from persons holding, or in process of qualifying for, Broadcast Operator's Certificate, for appointment as Technician.

Selected applicant will have prospect of advancement to Chief Engineer. Unfurnished flat available at moderate rental.

Apply in first instance with details of experience to G.P.O. Box 1914R, Melbourne.



388
GIANT
SIZE
PAGES

HERE IT IS—the 1963 Catalogue of Lafayette Radio Electronics Corporation of U.S.A. packed with 1,000's of interesting items for the amateur, hi-fi enthusiast, experimenter, technician, hobbyist, engineer, student, serviceman . . . includes many exclusive LAFAYETTE lines . . . fully illustrated.

SEND FOR YOUR COPY TODAY! USE COUPON BELOW OR WRITE.

LAFAYETTE ELECTRONICS, division of Electron Tube Distributors Pty. Ltd.
3A WELLINGTON STREET, PRAHRAN, S.I. VICTORIA.
Send giant 388 page 1963 Catalogue No. 630. I enclose 12/6 by Chq./M.O./P.N.
I understand 12/6 will be refunded with my first order for £10.

NAME _____

ADDRESS _____

STATE _____

A/23

BRIGHT STAR CRYSTALS

FOR ACCURACY, STABILITY, ACTIVITY
AND OUTPUT



Our Crystals cover all types and frequencies in common use and include overtone, plated and vacuum mounted. Holders include the following: DC11, FT243, HC-6U, CRA, BTG, Octal, HC-18U.

THE FOLLOWING FISHING-BOAT FREQUENCIES ARE AVAILABLE IN FT243 HOLDERS:—

6280, 4095, 4535, 2760, 2524 Kc.

5500 Kc. T.V. Sweep Generator Crystals, £3/12/6.

100 Kc. and 1000 Kc. Frequency Standard, £2/10/0 plus 12½% Sales Tax.

Immediate delivery on all above types.

AUDIO AND ULTRASONIC CRYSTALS—Prices on application.

455 Kc. Filter Crystals, vacuum mounted, £6/10/6 each plus 12½% Sales Tax.
ALSO AMATEUR TYPE CRYSTALS—3.5 and 7 Mc. BAND.

Commercial—0.02% £3/12/6, 0.01% £3/15/6. Plus 12½% Sales Tax.

Amateur—from £3 each, plus 12½% Sales Tax.

Regrinds £1/10/-.

CRYSTALS FOR TAXI AND BUSH FIRE SETS ALSO AVAILABLE.

We would be happy to advise and quote you.

New Zealand Representatives: Messrs. Carrel & Carrel, Box 2102, Auckland.
Contractors to Federal and State Government Departments.

BRIGHT STAR RADIO

46 Eastgate Street, Oakleigh, S.E.12, Vic.

Phone: 57-6387

With the co-operation of our overseas associates our crystal manufacturing methods are the latest.



DX NOTES

(Continued from Page 17)

JJV, YO7DO, and many others. (Your previous letter missed Dec. early deadline, sorry, Al.)

Ivor VK3XB comes to light with a long list of really good ones, wkd. in the last few weeks. 7 Mc. c.w., G3IMV, KH0KDD, CE1BD, H4K8H, VY2AS, GJAG, Y0KRN, G2MUV, UT-5AA, OET1, OHNV, DU7SV, VRL, HK0ZU, FJ2AE, YS10, 4X4HQ, H0B80, 5B4IF, KP-1400, DU7ZN, IZ1L, DU1GT, Y0Y0G, U4PFF, DJ3VXC (XYL), G5BZ, SM3AKW, OK2QX, CRAC, G3M0Q, SP8H0V, etc. 14 Mc. c.w., HK3KG, KC4UX, DJ7CZ, H1WC, S150, FEPO, AS7NE, U7KDD, U7B7V, VZ2MV, VP-ERG, VR2MV, S4ITW, ZEEJ, VY5AE, KG-4AM, etc.

Ivor, XYL, VK3KS, wkd. on 7 Mc. c.w., VS1FZ, DV3VXC (YL op.), VE1ZZ, DJ7CZ, and others. 14 Mc. c.w., UL7KDT, UDEKAK, UB-3G, G5AAE, K04AM, UQ0FF, VZ2MV, S4ITW, SM3AE, Y4RLOU, LZ1CF, DU10R, DL3EG. (Nice teamwork, let's have more notes p.s.)

Darrell L5041 heard some choice ones these past few weeks. They are 14 Mc. s.s.b. and between 800-1100 GMT. V81AJ, V68RE, V5-8CL, KCAUSG, KR8RN, KR3CP, KGA5A, GSKS, GA4UF, P7AA, SM8RN, AF5DC, OZ3Y, VRED5, YN1GM, KC4UX, KR00H, PYCME, DL15M, BY2CW, H0B8T, H4K8H, etc. 14 Mc. a.m., LUTHI, BV1USA, AC3AX. (S.s.b. reports always needed, so v'y my tks.)

Bev Davery, VK3JL, H.A.A. S. Townsville, reports conditions on 20 mhz as good around midnight and late afternoons. He wkd. on 14 Mc. EY1BUE, CE1AD, DU7FV, DU7SV, G5WPF, G13IV, SM61JU, UL7K8K, KR8BD, OH2BZ, VQ2WR, OH3UO, V2R2H, VU2KV, Z52RM, HSC1, Z55Y, H8GJ, H4B8F, KX0QC/KG, etc., and heard a large number of really good ones. (Tks, Bev, it's always good to hear what's happening in the tropics.)

Due to space limitation, it has been necessary to precis some of the above reports. Sorry (chaps.)

W.P.X.

Meet overseas mags. feature a W.P.X. Honor Roll. Such a list creates interest and competition. So how's about submitting your W.P.X. score. It is tallied by adding the number of countries wkd. to the number of areas contacted within those countries. Let's have a better response than last year's request. When sending in your notes or DX news, please include your W.P.X. score as well. Remember it is an Honor Roll and all claims must have QSL verification. Please indicate your section, i.e., c.w., a.m., s.s.b., or mixed.

SUMMARY

Radio Storm. During such a disturbance signals spread near or through the auroral zones fade out, sometimes entirely if the storm is severe. During this time it is best to concentrate on east-west paths in the daylight

hours and on north-south circuits during the morning and evening periods. Usually some band or circuit is workable.

Some of the VKs who helped this page along last year were 2QL, 2AMB, 3QU, 2AXK, 3ZA, 2AQJ, 3GV, 3ARX, 3AHO, 3HG, 2TL, 3AZD, 3Z1HR, 3AKN, 3ZMS, 4DO, 4XJ, 4BL, SRX, SRK, 5ZC, 5JE, 5MY, 5NO, 5NQ, 6SM, BRO, BERS195, L502, L511, L5065, L4001, L8021, L5041 and Rod de Balz. Let's hear from all you again, and others too, during '63.

PS—To facilitate matters, please mark envelope "Radio News".

W.I.A. D.X.C.C.

Listed below are the highest twelve members in each section. New members and those whose totals have been amended will also be shown.

PHONE

Call No.	Cer. No.	Call No.	Cer. No.
VK6RU	2 270	VK3WL	14 211
VK5AB	45 275	VK3ATN	26 204
VK6MK	43 286	VK4HR	12 192
VK3AO	23 284	VK4RW	23 184
VK4PJ	21 236	VK3BG	50 183
VK6KW	4 211	VK3WO	50 178
Amendment:		New Member:	
VK3BM	54 129	VK1JZ	61 180

C.W.

Call No.	Cer. No.	Call No.	Cer. No.
VK3KB	10 305	VK3RP	56 229
VK3CX	26 288	VK3FH	15 226
VK3QL	5 279	VK3BZ	6 222
VK4PJ	20 270	VK2AGH	71 220
VK3NC	19 261	VK4HR	8 218
VK6RU	18 258	VK3XU	48 213
Amendment:		New Member:	
VK3RJ	42 195	VK3APK	76 174
VK3ARX	66 190	VK3AX	86 136
VK3NQ	73 182		

OPEN

Call No.	Cer. No.	Call No.	Cer. No.
VK2ACX	6 300	VK3AO	76 262
VK6HU	8 259	VK3EG	3 257
VK4PJ	32 278	VK4ER	7 233
VK3MK	74 269	VK3BZ	4 231
VK3NG	76 265	VK3JA	42 229
VK3AGH	83 265	VK3WL	23 225
Amendment:		New Member:	
VK6KW	13 221	VK2AXK	89 102
VK3NQ	81 200		
VK3APK	82 190		

V.H.F. TWO-WAY RADIO FOR PRIVATE AIRCRAFT

Ferris Bros. Pty. Ltd. have announced the signing of a contract with Rex Aviation Pty. Ltd. to manufacture v.h.f. two-way radio equipment for installation in private aircraft, in particular the Cessna range which is distributed in Australia by Rex Aviation.

Developed by Rex Aviation engineers, the set has been approved by D.C.A. Ferris are confident that their experience in the manufacture of mobile-type electronic equipment will ensure that the product will meet all requirements.

The Rex Air Major consists of a transceiver and power supply unit, each separately mounted.

The transceiver comprises a 10-channel crystal controlled tx-rx operating in the 118-130 Mc. band. R.f. output power on full modulation of the transmitter is 4 watts.

The power supply is designed to operate and change over from either 14 or 28 volts d.c. without modification. Current drain at 14 volts is 3.3 amps. on receive and 4.5 amps. on transmit. A pair of switching transistors and silicon rectifiers provide efficient d.c. conversion. The audio output stage, which acts as a modulator during transmit, employs a pair of power transistors in push pull. It is incorporated in the power supply to keep the dimensions of the transceiver to a minimum and to limit the temperature.

Further details may be had by contacting Miss Hocking of Ferris Bros. Pty. Ltd.

S.S.B. CRYSTALS

Set of Five Gold-Plated Matched Crystals

Mounted in HC6U Holders
Suitable for 455 Kc. I.F.s.

Price £16-10-0 per Set
+ 12½% Sales Tax

Full details on request.

BRIGHT STAR RADIO

46 Eastgate St., Oakleigh,
S.E.12, Vic. Phone 57-6387

GRD DDP OSCILLATORS

FULLY WIRED AND TESTED

Well known American brand EICO. These instruments are exceptionally versatile, stable, rugged and compact units especially suited to the Amateur's and Electronic Serviceman's needs. Easy to hold and thumb-tune with one hand.

Frequency Range: 400 Kc. to 250 Mc. in eight overlapping ranges. **Coils:** Precision factory wound on polystyrene formers; coils are specially treated to prevent the windings from moving if accidentally knocked, etc. **Meter Movement:** 500 microamperes. **Frequency Indication** is by means of a rotating drum (housed inside the case) with 340° rotation; scale length is 3½" long. **Circuit** uses Colpitts type oscillator with improved grid current stability over the tuning range. **Tuning:** Tuning condenser is equipped with a 1:7 ratio planetary drive. **Power Supply:** Self contained transformer operated selenium rectifier. **Dimensions:** 2¼" high, 2½" wide, 6½" long.

PRICE £29/17/8 complete, including Sales Tax

All goods sent by Certified Post. Be sure to include your FULL ADDRESS and Money Order or Cheque with your Order. Easy interest-free terms available if required. Available from—

THE RADIO EXCHANGE CO.

SHOP 1A, ALLAMBIE HEIGHTS SHOPPING CENTER
40-7844 ALLAMBIE HEIGHTS, N.S.W. 40-9604
Country Clients, Please Note After Hours: XM 7691, XJ 6596

The New Issue of 1962-63

CALL BOOK

is now available

ORDER YOUR COPY NOW!

S W L

OH0, KL7, ZD8, ON4, LZ, FF8, VP8, XW8, 5H3, WO

Sub Editor: J. M. (Mac) HILLIARD, WIA-L3074

57 Gardenia Street, Blackburn, Victoria

ADDRESS CORRESPONDENCE FOR THIS PAGE DIRECT TO THE SUB EDITOR

Hi there fellow S.w.l.'s, it has fallen my lot to present these notes to you. I would like to thank our retiring President and Sub-Editor Bob Young for the excellent job that he has done.

The starting off point for many of the Hams of today begins in the S.w.l. ranks, but why do so many of the Hams disregard the average S.w.l.? I admit that many of the Amateurs give much assistance to the newcomer. However there remains a large number who scorn at the S.w.l.

The practice of sending bad reports no doubt could be a contributing factor in conveying a poor impression of the S.w.l. in the minds of many Amateurs. But surely this is no reason to condemn the S.w.l. in general.

Recently a local well known Amateur here in Melbourne, who operates on s.s.b., was heard in one of the most glaring cases of ill manners that your scribe has ever heard on the Ham bands. The said Amateur was in contact with a W station, who was, by the way, 89, when another Melbourne station broke in. This in itself was bad enough. But then the chap that had been working the W promptly started yarning with the local and just left the W out in the cold without making any further reference to him. Surely this is one of the poorest cases of bad manners ever heard on the bands.

Remember chaps, this page depends on you and I am looking forward to hearing from all of you. All Interstate correspondents will be answered and also locally where required.

VICTORIA

At our Xmas wind-up, we held a special meeting with the prime purpose of electing a new President, another Vice-President and a new Sub-Editor. The election resulted in Maurice Cox being elected to the chair with

Bob Young as Vice-President, and yours truly as Sub-Editor. Bob was forced to resign from the chair and also as Sub-Editor due to lack of time.

Much discussion took place as to how we can increase the membership of the Group. It was felt that if members had more to do in the Group that more interest would be forthcoming. Many of the younger members cannot afford to buy expensive receivers and it is to these younger members that we must encourage. At the conclusion of the meeting we all had a few cold and soft 807s.

The big event of the year will soon be coming off and of course that will be our Convention at Ballarat, which takes place over the first week-end in March.

Our President, Maurice, has been flat out in the Ross Hull Contest. However, he will not have things his own way as Ian Thomas and Bob Young have not been idle during the Contest. David L3125 has just erected a long wire which is 120 feet long and it is pulling in the signals in fine style. His hearing aid is a dual wave receiver. Very pleased to hear from you David and will be looking forward to receiving further news from you.

QUEENSLAND

Only news to hand from VK4 this month comes from our good friend Afton Westcott up at Atherton. Afton has been on the sick list for several months. We are all sorry to learn of your troubles Afton, and wish you a speedy recovery and hope you will soon be back amongst the DX. How about some of you other VK4 boys dropping us a few notes of your activities now and again?

NEW SOUTH WALES

Our old Buddy Chas. Abernethy is going well in the Ross Hull Contest, and my spies

tell me he has over 1,300 points. Best of luck to you Chas.

I would like to remind you all that I must have all correspondence for this page no later than the last day of each month.

What has become of you fellows in VK8? Apart from Peter Drew, we would not think that VK8 existed as far as S.w.l.'ing was concerned. So what about it, you chaps?

Remember this is your page and it is up to you to provide us with news of your activities. But unless you do this, we can hardly be expected to provide news out of the air.

Well that is all for this month, so 73, Mac Hilliard.

DX LADDER

Countries	Zns.	S.s.b.	W.
Conf. Hrd.	Conf. Hrd.	Conf. Hrd.	Stat.
E. Trebilcock	277	282	40 — — 50
D. Grantley	111	250	38 16 95 34
A. Wencott	94	159	31 9 107 11
M. Hilliard	70	214	33 12 122 11
M. Cox	61	230	29 27 135 16
C. Abernethy	44	85	27 — — 14
N. Harrison	38	92	27 — — 29
P. Drew	33	180	19 7 93 11
I. Thomas	29	134	18 8 88 11
P. Fields	26	133	— — — —
D. Jenkins	10	144	7 — — —
H. Burger	6	185	5 1 19 —

NAT. FIELD DAY CONTEST

9th and 10th February, 1963



UNIVERSAL SOUND

DYNAMIC MICROPHONE

Model 603



A Product of Italy

Omnidirectional.

Output: —50 db.

Response: 50-12,000 c.p.s.

Impedance: 50,000 ohm, 250 ohm or 60 ohm.

Dimensions overall: 40 x 40 x 98 mm.

(1-9/16" x 1-9/16" x 3-13/16").

Accessories: Table base.

Model 603 is a Dynamic Microphone ideal for music, speech and particularly magnetic recording. Can be used on stand or on a small table base.

Smart square shaped aluminium pressure cast case with stainless steel wire mesh.

Sturdily built and beautifully finished.

Impedance can be easily stepped down from high (50,000 ohm) to low (60 or 250 ohm) impedance.

Retail Price: £14/0/0
Plus Sales Tax £1/9/2

Marketed by

ZEPHYR PRODUCTS PTY. LTD.

58 HIGH STREET, GLEN IRIS, S.E.6, VICTORIA

Phones: 25-1300, 25-4556



FEDERAL AND DIVISIONAL MONTHLY NEWS REPORTS

(SEND CORRESPONDENCE DIRECT TO DIVISIONAL REPORTER NAMED AT PARA. END)

FEDERAL AWARDS

During the past year W.A.V.K.C.A. awards Nos. 196 to 230 have been issued to the following:

- WEDQH GIBZO VEIBQ JASAA
- W2NU GQDQC UAAGF JA7AD
- GMGMD GGVQ UAFZA WHIGT
- UCJAA FVWIB JAFVH
- G2FPO ZLIARY KW0BQ ZL3VI
- XEICV ZL3OB WHQBA UA9VB
- GRGM WIEQO VSBEC VU2AJ
- APMS APBCP WSMCK W3RZL
- KUYF WIUOP JALAJU

Australian D.X.C.C. Countries List in "A.R." January 1963: Amend "Pakistan" to read "East Pakistan" on fifth line.

A. Klesick, VK3KB, Manager.

— * — * —

NEW SOUTH WALES

The Xmas meeting of the N.S.W. Division was held at the Wireless Institute Centre on Friday, 14th Dec., and the attendance was so good it was a battle to find enough seating accommodation.

Essential business was disposed of as soon as possible and the meeting handed over to Alf BZW who operated the projector and put on a two-hour show of films, the feature film being the "Space Age"—a documentary film of the recent orbital space flight of Major John Glenn. Portions of the film showed pictures taken from the capsule in orbit.

The President (Max ZMP) moved a vote of thanks to Alf for his capable handling of the projector, but more especially for the fact that Alf has donated the whole 18 mm. projector and sound equipment to the Institute.

After the films Max wished everyone a Merry Xmas and closed the meeting for refreshments served from the kitchen under the supervision of Gordon ZAG.

Another Xmas Party was held by the Griffiths Radio Club on Sat., 8th Dec., at the residence of the President (Freda ZSU). Visitors present from Hilsilton, Tabbita, Leeton and Narrandera. Blind fold x hunts, dancing to bagpipes and a barbecue were held. The lawn and there was a buffet table well stocked. Musical items were supplied by Mrs. Savage (XYL of 2ACB), Doug and Paula (harmonics of Freda ZSU). Approx. 80 Hams and friends attended the function.

The last Council meeting for 1963 was held on 20th Dec. and the Council appointed Pierce ZAPQ as organizer of the forthcoming Federal Convention to be held at the Wireless Institute Centre over the Easter holidays. Pierce has a big job in organising such things as the Federal Dinner, accommodation for delegates, transport to get the delegates to and from the meetings, meals, reporting facilities, etc., and he would be pleased to hear from anyone who can assist him, ring Pierce at UT 6125. The Education Officer, Harold ZAAH, had a spare night over the holidays so he knocked up another tape titled "A Spare Night V.H.F. Aerials" by ZAAH. This tape runs for 65 minutes and is illustrated with 32 slides. For particulars, contact Harold.

It has been the custom from time immemorial, to set aside the February meeting for the v.h.f. boys, so we are looking forward to a good feature by the v.h.f. and I.v. Group, 23, ZVL.

HUNTER BRANCH

The Christmas meeting of the Branch was held on 14th Dec. and, after the shortest business session on record, the 22 members, associates and visitors present settled down to an interesting evening of colour slides presented by Bill ZXT. These featured his recent trip to the Far East and were liberally sprinkled with pictures of particular Amateur interest. At the conclusion of the show, the festive entertaining items, l.v. and translator radio-phones were displayed, and used. Both created quite a deal of discussion centring mainly on present day festive entertainers. The night concluded with the usual ragchew and wishes to all.

During the holiday season activities have been much as usual, but the v.h.f. boys have been taking particular care to get the 50 Mc. gear in trim for the excellent openings which have been appearing on that band. It is even re-

ported that ZEMO wishes to have a telegram sent if anyone wants to contact him on 144 as he is so busy on 61. Others on the 50 Mc. bandwagon are Ian ZEF, ves ZEDN, and Stuart ZAYF, to mention but a few. Still in the v.h.f. spectrum, it is interesting to note that there has been an upsurge of 144 preservers in the coastal city. Peter ZALY has a brand new high power rig almost ready to go and when I say high power, I mean just that. He burned out a 9.5 amp. 61 meter in the dummy load while testing the gear! As for the other in the 2PZ vicinity, things are moving, but slowly. Chris is waiting for his licence arrives. Len is building but how close to being on the air is not known.

Two more members have been notified of their success in the limited examination. They are Bill Sinclair and Len Daley. Bill tells me he is ready to go on the air as soon as the licence arrives. Len is building but how close to being on the air is not known.

Out by the lake side is one very proud Amateur, Jim ZAH. He has been notified of his winning of a 1000 watt licence. Jim is a little more than means another attractive certificate to grace the shack wall. In addition, he has all the cards ready for D.X.C.C. which is really fast work considering the short time Jim has been active during the present spell of operation. Another consistent signal is the plea from Bill ZEL for a 1000 watt licence. This means crane. Bill is having some trouble getting labour to install the new piers for the railway and is thinking of borrowing a few sky hooks and some rope.

Nell ZECU hopes to be out of hospital and back on the job again soon and it is hoped that you will hear from her again. Another member on the sick list is Ern ZEP. All the best for a speedy recovery and return to the old firm where, by the way, the thing was a bit better. Lionel ZCS returned. It is said the water supplies are now in very good hands.

Rodney ZCN has a new 18 over 10 long term for 2 on 144. The new rig is as good as is Ron ZASJ, now a regular 2 mx max. Another seldom heard signal on 2 is Ron ZAAI, while Greg ZEKW is having some trouble with his 50 Mc. rig. He finds this is wanting to do with the anchorage point for the beam. Varley ZSF is now on one band at a time, which is more than I can say for the signal from this QTH, so progress is being made. Les ZRJ apparently has had a great deal of success with mobile operation in VK3, so ask him about it at the next meeting.

Gordon ZZSG is busy with audio troubles, but still manages to get a signal out, but I haven't heard Tony ZZQ of late, and he says he has changed employment. Bill ZXT has little time at this end of the year and is still busy dispensing with Bob ZAGR although it's quite at home now since number 1 is on left for Narrabri. Norm ZZNIF still is trying to get some signals out of the AMR300 and has something—V.H.F. 20 Mc. re-builder rig so you can see that 1963 has been good all round.

It'd all like to see you at the next meeting which will be held at the Newcastle University College on Friday, 8th Feb., so why not come along. The lecture room is very large and we'll keep a chair for you, 13, ZAKX.

VICTORIA

Possibly one should start by apologising for late notes the last two months. Liability for me, some kind person supplied notes on the State Convention, and as I was not at the time, I cannot give you a more detailed account of the Dec. issue. The Dec. Council meeting was too late for Jan. notes, and at this late stage I'm rather hazy about what took place. The room was made for the re-housed, in fact the new bookcases should be installed and in use by now. The test bench project appears to have come to a stop, due to the resignation of the moving force

behind it. This matter will probably be fixed early in the new year. The Moon Bounce project is a dark secret (at least to me). Can anybody produce any info.

Council will next meet at the end of Jan., but as I will not be there, perhaps our Publicity Officer will send some notes to "A.R." What about it Harold?

The Institute suffered a sad blow in the death of Bill ZTX early in December. Bill had a licence since 1945 and he was back about 1912. For the last five or six years he had been closely associated with the Publications Committee as circulation manager. 3BN, ZAFJ, 3OM and 3AOM were among those who attended the funeral.

Now that these notes are being typed, I don't feel very sorry about the printer. As they can now be read, Parsons will have to have his space reduced in my favour. After all, I am a friend of the whole committee, etc., etc., and I don't want to show him there are no hard feelings, I'll publicly thank him for his Xmas Greetings and at the same time wish him all the best for 1963. I'll even go further and tell him there are strong indications that his old "Arch Enemy" will be heading for the City of Clubs during February, and when last seen was checking his array of lethal weapons.

The friendly net (144.86 Mc.) is growing with the release of further carphones, as is now spreading into the country areas. They now form a solid core to W.I.C.E.N. Fortunately their services have not been required for any night in W.V. during this summer, but there is still a couple of hot months to go. Plans are in hand for similar nets on other frequencies. Has anybody got a radio for action one night in mid Dec., when a boy was missing in the Dandenongs. Several members were in the area assisting and the boy was found before full scale operations were needed.

Heard by the grapevine that communications by the people patrolling the Nullabor during the Empire Games were not all that could be desired. Has anybody got a radio for action? Could make an interesting article for the mag.

Saw ZALK recently and sorry to say, he has been far from well. Maybe too much effort for 2 on the network for 3WT, ZAKX, another who has been on the sick list, but has since been heard operating mobile marine in contact with the heir to the family fortune, ZAAA, who was operating mobile. Talking of sick lists, what is wrong with the Ballarat air.

CENTRAL COAST FIELD DAY

will be held on

17th FEBRUARY, 1963

at the

GOSFORD RACECOURSE

Be on a winner—be at the best field day in VK3.

Reg Brook, VK2AL, Hon. Sec.

N.S.W. DIVISION, W.L.A.

NTH. COAST & TABLELANDS

ZONE CONVENTION

will be held at

URUNGA

during Easter Week-End

12th to 15th APRIL, 1963

144 Mc. is hunt, 40 mcs. to hunt, all band, scramble, general, entertainment. Accommodation of all types available on application to Mr. J. Walters, C/o, Ocean View Hotel, Urunga.

Most of us, at some time or other, have been approached to "Just have a look at my television and tell me what's wrong with it." I'm just a TV addict, but I can write a novel variation. Being by nature a shy but helpful type (PanSy won't think so.—Ed.), reluctantly toddled off to have a look at the monster. Now if ever you've climbed out of the works of one of those things, you'll find a little more than a standard repairman's understanding by watching, you'll know what I mean. Possibly somebody years older than myself (like 5PS) could handle the situation, but not me! I couldn't have even changed a tube. Can anybody tell me if this live of heaven's sake, why do I have to live? It makes me a radio astronomer? Gosh,

MIDLAND ZONE

I have no apologies to offer for the non-appearance of the Zone notes in the Jan. issue of "A.R." as they were in the post on 6/12/19. What happened Ed? As notified in Nov. 1968, the Jan. Zone closed on 1st Dec. 1968. Activities on Zone hook-up and reasonably favourable and on the increase. There have been some DX break-throughs on 6 mx of which our President (Don Carr) has taken advantage of when he had the opportunity, as well as operating on the 2 band. I am not afraid of not being well informed on the activities of Zone members generally, but due to the holiday period this is to be expected.

My own activities have been confined to operating on 20 mX DX and some local 40 mX QSOs. 3AQU is also active on 20 mX DX, operating from Kyneton with a Q4 54 signal in Castlemaine. Please note, your copy of the minutes of our last meeting held at Bendigo will be forwarded together with your next meeting notice in order to reduce postal costs. Our funds just won't stand two despatches. 73, SMD.

EASTERN ZONE

Ken (ex 3ZNB) and Ross (ex 3ZAQ) now have their full call signs. 3OI (Moe) and 3NS (Warrigul), both stations operating initially on 40 mX. 3AMS at Foster and Martin 3AMV at Warragul hope to come on in the next few weeks. Jack 3AJK is still winning more countries on 14 Mc. phone; he now has over 20 countries marked up. The v.h.f. boys have been working their fair share of DX.

The Eastern Zone members are quite keen in setting up an emergency network throughout the Zone. The v.h.f. boys are buying f.m. carphones, two are already installed. Stations willing to operate on 3550 kc. please contact David 3NY

Our Xmas party at Alf's went off extra, again. Best wishes and DX to all Zone members for 1963. 73, 3ZCG.

WESTERN ZONE

Among those representing the Western Zone at the State Convention in Ballarat were Keith JATS and Wilson JAFU. Wilson didn't come to the convention, but he is a "strong" person for "most miles travelled." Keith JATS, just out on the Horsham side of Murtlo, should soon be sporting a new "strong" person. He is at present preparing to erect a second 60 ft. steel tower. With a half wave on 80 slung between these, he will be able to work the Western Zone. He has now completed a low power emergency transmitter operating from a 12v. battery, a permanent addition to the shack "just in case". Hams to help place his new 40 ft. windmill tower in the vertical plane. When this is done the tower will be dorned with a cubical quad on the 70.

3AZ, Hugh McLachlan, better known as Mac,
is now residing in Hortham. A s.b.m. man
for many years, he has been in the 30 and
m.v. Vln 3AEQ, a regular on the weekly Zone
hook-up, is now approaching the busy time of
the year. He will be absent most Wed.
days until the end of the week. As 3AEQ was
formerly of Shepparton, is now living in
Ararat. Welcome to the Western Zone Nev.,
and you p.m. netting. Keenly interested
in the present difficulty working DX on
the h.f. bands due to heavy QRN of the man-
made type. Seems as summer approaches the
situation is becoming progressively worse. A
lot of trouble is the h.v. S.E.C. power mains.
Perhaps a decent showing of rain will cure
things. Chas. Bill BAKW about to have
his S.B.M. man's Hope Chas' troubles
don't frighten you, 3AUV

This is the first rotation of Zone notes correspondents on a roster system as decided at our last Convention, so in fairness to the next in line, let's see a zone-wide roll up at all future hook-ups. T3. 3AFO.

QUEENSLAND

Well the wheel has spun around again and picked me up for the second time. I thought we had trucked out when Don Marshall took over our "A.R." sub editorship and news service, and so we had, but Don is busy building a bower for his bride to be and won't be with us for a while. Thanks for your help Don and all the best to you and your YL. Who is going to do the job now? I'm not a 4PR that can take several jobs at once. Get off your ——— some of you chaps and have a go. What about a country member for a

Talking about country members. At time of writing Claude 4UX came down through the rain to spend a week or two in Brisbane. Frank 4FN was about though I didn't contact him and Basil gave me a ring one night but I didn't meet our Mt. Isa mobiler 4JC; next time hope they'll be easier to handle. Some members shake themselves know even though it might only be over the phone. That's not bad is it. I guess most of our country correspondents are on holidays as little in the news line has been received here. See that some comes by the end of the month fellows.

What action have you taken on the Suite Council nomination form in "QTC"? If the person nominated can forward or have forwarded a few words about himself it will help country members, in particular, in voting. e.g. number of years a licensed W.I.A. member, offices previously held in the W.I.A., if any, occupation, age, etc., but it is up to the person concerned to supply this information.

Please read the requirements for nomination as several quite unacceptable forms were received last year.

Has anyone given thought to what should be done if sufficient nominations to form a Council are not received? Should the Federal body take over? Give a few more thoughts to the formation of Council and do something about it.

By now you should have Pat's (4KB) notes on the constitution and realise it is quite a problem, taking up real time, to find a good solution.

Glad to see Jan. "A.R." with a couple of articles of VK4 origin printed. Should be more of it. (Always pleased to receive articles. —Ed.)

I wonder if we will have passed our membership of 400 by the time this goes to press? Don't say it can't be done—a lot of people thought it a great joke that we thought of winning the R.D. Contest, but we ran pretty close. Oh for those 12 or 14 logs—how valuable they would have been. Where's my handkerchief.

Have you forwarded your Jamboree-of-the-Air report? Better late than never. A very nice card and letter of thanks to hand from Kallangur Group.

Ron Rees, ex 2DR, ex 4DU, now 9DR, is now radio officer at Christmas Island in the Indian Ocean. Don, who will be coming back to Amateur Radio after 23 years, was once Secretary of the VK2 Division when Bill Moore, Jim Corbin, Morrie Myers, Peter Adams and others were on the committee at that time. Don has a 200 ft. tower and a 150w. tx ready to go.

In the meantime have you any radio courses, text books, old copies of "CQ," "QST," "A.R." etc. for a radio club technical library that Don is assembling in conjunction with a radio club he is forming on the island? Contact Box 6383, G.P.O., Brisbane, and we will give forwarding instructions.

On 30th Nov. one of our most interesting visits was made to the Brisbane City Council Standardising Laboratory at Mayne Junction where most of the commercial measuring instruments used in Queensland are calibrated. Most of the liquid measuring vessels and pumps to too many decimal places for the average Amateur, but the various demonstrations, including c.r.o.s., etc., were all very worth while. Thanks to Mr. Gow, engineer-in-charge, and to the B.C.C. for the excellent support provided.

Well I've been stricken with the B.C.C.-S.E.A. merger and laryngitis apart from personal problems, but I would like to be portable for the National Field Day. I'll be trying. Will you be in it? Let us see a few more VK4 notes this year.

Sam 4CZ is getting about again and by now I hope is back to normal health. Sam is now with the S.E.A. Bill Jehn, our s.w.l. registrar, had such a good time in Adelaide he didn't even have time to look up SPS.

Thanks for giving Alf 40L a call when he is running the 4W1 session on Sunday morning. Rick 4VR usually carries on after the news on 20 mx band and would welcome a call. What about it hornheepers? If you can't stay home for the main hook-up on 40 mx, just drop in on your car guys when you can, a few just like to know you are about. You can always get Alf around 7145 before 6900 hrs. and pass on any items of interest—he will appreciate same.

By the way, in the first call please try and limit yourself to your call sign and keep reports and business to the second or third call. It's sure more will participate in the first call in if there is no delay. 73, 4PJ.

TOWNSVILLE AND DISTRICT

As these notes will be the first for the New Year may I take the opportunity of wishing each and everyone a Happy New Year and the plots I hope that you all have a better one. I am listening to the boys on the Kookaburra Session and from all accounts the bond on 7 Mc. is not too good as they are experiencing difficulty in hearing each other. While on this subject, the old cry what has happened to the boys on 14 Mc. on Sunday morning at 11.00 AM. I had a hook-up at times 4VR and 4ZM are heard and seems I cannot always break them.

No advice from my spy on the Lower Burdekin as to what is happening down there. The boys are not in Cairns, but the notes. Locally not much doing on the air but recently happened to hear John 4DD, and other than Charlie on 7 Mc, it is pretty dull listening. Bert 4LB don't rate a mention as we can almost hear each other if the windows are open. Basil on 7, down in Cairns, just came in from the family row in the southern States for nine weeks sighting and reports that the Z boys in Cairns are making hay and the 4 boys in Melbourne are making hay south and playing around the town on 144 Mc, while Bill 4ZEE has worked into VK5 again and has quite a number of QSOs with the boys down south. 13, 4RW

SOUTH AUSTRALIA

The monthly general meeting of the VK5 Division for Dec. was held in the clubrooms to a capacity gathering of members, together with an increased number of the female sex. The night took the form of a Xmas Get-together and was the usual great success, judging by the reactions of all present, and must have pleased all those behind-the-scenes.



SOLDERING TOOLS

This range of precision made soldering tools and equipment, widely used overseas, has been designed and developed to facilitate the fastest and most efficient soldering of standard and miniaturised radio and electronic equipment.

Approved Mains Voltage Tools:


- No Transformer required. Supplied for all voltage ranges from 6/7V. to 230/250V.
- Instant CORRECT Temperature.
- Light weight, perfect balance.
- Low Loading, and cheap to operate.
- Long life.

Further information from Manufacturers:—

ADCOLA PRODUCTS
PTY. LTD.

673 WHITEHORSE ROAD, MONT ALBERT, VIC.

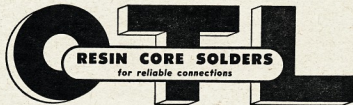Telephone 88-4351. And all principle radio parts supply houses.



G. T. LEMPHIRE & CO. LIMITED. Head Office: 27-41 Bowden Street, Alexandria, N.S.W.
and at Melbourne • Brisbane • Adelaide • Perth

LOW DRIFT CRYSTALS

FOR
AMATEUR BANDS

ACCURACY 0.02% OF
STATED FREQUENCY

3.5 and 7 Mc.

Unmounted, £2/10/0

Mounted, £3/0/0

12.5 and 14 Mc.
Fundamental Crystals,
"Low Drift,"

Mounted only, £5.

THESE PRICES DO NOT
INCLUDE SALES TAX.

Spot Frequency Crystals
Prices on Application.

Regrinds £1/10/0

MAXWELL HOWDEN

15 CLAREMONT CRES.,
CANTERBURY, E.7,
VICTORIA

THE NEW "A.R." LOG BOOK

IS NOW AVAILABLE

Larger, spiral-bound pages
with more writing space.

Price 5'6 each
plus Postage

Obtainable from your Divisional
Secretary, or W.I.A., P.O. Box 36,
East Melbourne, C.2, Victoria.

responsible for the arrangements. Last year was the first time that any XYLs or YLs attended and since then their numbers have increased considerably, and as I said last year in the notes, it is becoming increasingly apparent that at some time their numbers will reach the point when it will have to be considered a social event and not just a get-together of the boys. Quite possibly there will be one of the YLs who will come along with this, but in our democratic set-up the majority must prevail, even if the skies fall during the change-over to the YLs.

Our President (John 5JC), unfortunately, could not attend owing to being in hospital for the purpose of having a few more d.b.s. added to his hearing, and Phil 5NN, Vice-President, did the honours for the evening, to good purpose too, if I might be permitted to say so, and declared the meeting open before the YLs. Business being attended for the night, the entertainment commenced and three excellent films were screened, and judging by the applause at their conclusion, were much appreciated by all present. QSL cards were then distributed by George 5RX, and at the same time the tables were set up, loaded with goodies prepared with loving care by Marlene and Christine, the XYLs of Brian 5CA and Geoff 5ZCQ. May their shadows never grow less.

Well, that's it gentlemen, once again the "Xmas Do" has come and gone, and once again the same old helpers did their annual chores. The thanks of the Division are theirs, and if they don't get their dues on earth, then let's hope they get them in Heaven, or anywhere else they might be directed to. Oh, and before I forget, to those ill-mannered and coarse types who suggested the SPS household would be living high for the next few weeks so that one of goodies that I carried out to my car at the end of the festivities was delivered, as is our custom each year to the St. Mary's Home for Orphan Children. The Matron of which sends her grateful thanks to the members.

To all of the gang who hopped in after the rats had cleared away and the place was swept and dusted, Council extends their grateful thanks, the same goes for anybody who assisted in any way. Nice work fellows. Oh, by the way, the attendance was around the 150 mark—not a bad roll-up for an organisation that has been described in some quarters as "dying on its feet".

Incidentally, this meeting was the last to be held in these club rooms and for the future the meetings will be held in the Builders' and Painters' rooms on the corner of the street on the fourth Tuesday night in the month, instead of the first Tuesday in the month as of yore. This change of date will probably cause some confusion, but I am sure that the members who have formed the habit over the last 40 years or so, but the VK3 Amateurs are right on the ball with such a transition, and it goes without saying that within the next four or five years or so, only a couple of them will still be turning up on the first Tuesday night as usual, but still comment "Why doesn't someone tell me these things"!!!!!!

I have received that long-awaited photo of the recent gathering of the clan at Crystal Brook recently, and I am glad to state that I would suggest to the Publication Committee that they put on their dark glasses to examine it, because it is a most interesting and a number of desperadoes gathered in one spot at one time would be hard to find. I never slept for three nights after merely stealing a glance.

The Port Pirie Amateur Radio Club held a meeting at the home of the Secretary (Bruce 5ZQZ) recently, and a number of new members were reported, including also a new member and two interested visitors. Inspector Bruer, of the local constabulary, came along and was highly interested in what was on Civil Defence, and later nobly withstood the bombardment of questions from those present. A very enjoyable evening was spent with the aid of plans are going ahead for the schoolboy instruction. Bert 5EQ is showing the lead in this by organising a film show to be held in the school hall on the 23rd of the month. Projectionist. Carting coils to Newcastle for film. Designs for the QSL card for the Club will be ready in a few days. The new XYLs, some rude, some coarse, are being received. It is expected to find something which will appeal to all tastes (probably that 'rain going up and down the street again!'). Thanks for the news, Bruce.

A real old-timer in Roy 5AC was heard recently portable from Wellington. He was reported to be a very old man, and was said to like to own up to, and when he retired he joined up with a well known brewery in our fair city, and he was said to be a very old man, a contact one day on 7 Mc, that he was never

happier. Nice to hear you Roy, what about coming to a mod one night?

Tom 5TL still spends his Saturday afternoons at the local rifle range and if it is to be believed, has not lost any of his cunning in hitting the target. He and I were once fellow members of the Postal Institute rifle club, as was Inky 5WF. Incidentally, there is not a word of truth in the oft-repeated statement that I once scored a bullseye at 500 yards by throwing the rifle at the target!

Tom 5QL at the moment of writing is enjoying a well-earned holiday and expects to be operating portable a.m. Slumming I expect he would call it. So far I have not heard him but I am sure, but should Peter so with hard put to keep the sneer out of my voice. A.m., how low can one get!

Heard Joe 5JO on 7 Mc, the other Sunday morning. His XYL, Nellie, was doing a good stick on the mike and was attracting all the stations on the air, like flies to a honey pot. They both seemed excited about their coming Xmas tour around the country side, complete with portable set-up and all mod. cons.



Some of the Amateurs present at a gathering at Crystal Brook recently. Left to right: Back row: VKs 5ZMK, 2nd operator at 5RJ, 5BZB, 5SL, 5ZBI, 5CO, and 5WO. Front row: VKs 5X-5VM, 5NW, 5EL, 5EB, 5AP, 5EQ, 5ZJM and 5EN. Also attended: VKs 5FM, 5ZKE, 5YA, 5DS, 5ZAH, and 5LL.

Jeff ex-5LZ5K, from Napier, N.Z., recently passed through Adelaide returning from the Empire Games. Having now toured VK land by car, he was en route to Sydney to embark on a tour of Europe and Africa, etc. Many of you who are reading this will remember his XYL Peta (5LZABJ), unfortunately now a silent key drowned and heavily surf in attempting to rescue her brother-in-law. It is of interest to know that the Napier Chess Club, of which she was President, and the Radio Club of that district have erected a clubhouse in the centre of that city as a combined memorial. The new clubrooms house the local emergency network control station, now operating under Peta's old call sign—5LZABJ.

The Woomeera Radio Club, 5WC, has at last moved into its new clubrooms and with the advent of "Beau" new gear, also become very active again. Membership and interest is steadily increasing, although the old stalwart Bern seems to have given up any radio in favour of playing the organ. In fact, an electronic version is being planned. Trevor, the Club President, was quite thrilled to find that the first ex he ever had worked on, Ian 5QX is vainly trying to talk him into building a modulator to keep it company.

Eric 5AVS has not been on the air much since he found himself an XYL, but his little tx still does sterling work, especially with the 5CQ. Ask Ian, he will guarantee it. Keith 5EP puts in an occasional appearance at the 5WC clubrooms and John 5EV still cannot get rid of the job of Secretary and is kept very busy in that respect. He still finds time, however, to cover himself in grease and perspiration delving into the mysteries of internal combustion engines.

Ian 5QX was down in their fair city for his annual holidays and managed to make the Xmas "Do", although he was leaving for Woomeera next morning at 4 a.m. or some such outrageous time. To get to my right

side he admitted to listening to the Best Broadcasting Station in VK on his way down and to cap it all, he called in to see me at the station. What more can I ask?

Tom 5PS was also at the Xmas "Do" and together with several other a.s.b. devotees, excelled himself with the soap and water at the washup after all the white ants had gone home. He still being bothered with strangely trouble, and has almost reached the stage of having the bullet, no cartridge, removed.

Well, one certain paragraph each month in these notes has now been taken away from me. Yes, with pride and due modesty, I can now announce that my Worked Elizabeth Award arrived over Christmas, some nine months late, but nevertheless welcome. Despite all the insinuations, the coarse suggestions that I was a "Ring-in", the threat to put the application before the F.B.I. and but not least, the cruel inference that some of the stations I named had never heard of me, I now have the award framed on the door of what is known among my cohorts as the "Single Sideband Room"! ('Tis said in VK3



that the award was created specially for PanSy because his signal cannot get much further than Elizabeth—Ed.)

Luke 5LL, back from his trip around VK1, has been in the club a few days when we went down with a stomach upset and had a bad week or so of it. Quite taken up with VK1 and its points of interest, but cannot help but feel that a lot more publicity could be given to a number of very interesting places and buildings throughout VK1, which take some of the credit for the success of the club. However, my spies reported that he and Harold 5PW were at the North-Western Zone Hamfest, but as no mention was made of it by the scribe for that area, I can only assume that my spies were leading me up the garden path.

Everybody at the moment is trying to get on the bandwagon of the Youth Clubs, and I feel that we in VK3 are apt to forget that the Association of Methodist Radio Amateurs and Clubs (SBA) has been in existence since July 1953. Started originally by Howard 5XA and John 5D at the request of the Rev. J. F. Ashman, the club still bring nobly help by Joe, who is the teacher and leader of the boys whose ages range from 9 to 14 years. Howard unfortunately had to give the job away but did yeoman service for some years. The club is the only member society of the World Association of Methodist Radio Amateurs and Clubs whose founder and secretary is Arthur W. Shepherd G3NGF. Nice work, Joe.

Carl 5SS and Frank 5MZ, the terrible twins, noticed at the Xmas meeting, and both seemed in the pink. Their parting shot to me as they left was that they QSO at different times these days, just to trick me. Fat chance! The 5EL tells me that he renewed acquaintance with Des 5DK (ex5DK) whilst in the Apple Isle and found him well and contented. Des wished to be remembered to all of his one-time VK3 friends.

Heard Rex 5KY and Reg 5BR having an old-time QSO on 7 Mc. during New Year's Day afternoon. By an old fashioned QSO I mean a QSO in which both sides are as natural to listen to as if they are in the same room, and with an entire absence of unnecessary technicalities. They were on for some time and discussed a variety of subjects from New Year resolutions to proposed shack renovations. Very easy on the ears, I think, it wouldn't get either of you a Nobel Prize for scientific discussion, but it sure was a pleasant treat.

One of my female spies, a seductive bit of the doings, informs me that Jim 5JK is disporting himself in a new car. So far I have not caught up with him, but something whizzed past our QTH last night with a loud foot-toe-toe, and if that was not our debonair champion, I think I need check my glasses.

By the way, my little paragraph regarding Jim 5JK being a clarinet player of note, foxed out the fact that Rex 5KY used to be a member of the combination, playing the saxophone and doubling at times on the squeeze-box. I might have my instruments mixed up a little, but at least two of our members have been hiding their light under a bushel.

Received a very unexpected telephone call from the Dept. of Civil Aviation this week and was quite surprised to hear a charming young lady ask me from the other end of the line, "Did I represent the radio magazine 'Amateur Radio' in Adelaide?" Feeling a little libel actions, unpaid debts, or possibly recriminations from the Victorian Duxstmen's Union re the radio magazine, I merely asked her to call again. She said, "Well, I have some slight dealings with them. What can I do for you?" Well, to make a short story longer, and thus upon the new year of '54, it appears that D.C.A. have heard of some conversation regarding the conversion of ARTs contained in some back issues of "A.R.R." and although they had contacted all booksellers, newsgaters, libraries, etc., etc., for back copies, they had no luck. Well, to make a short story even longer, however, I was able to send them 11 of the back copies they required, to the mutual satisfaction of all concerned. So there you have it, the famous "A.R.R." back copies. The Publications Committee might consider it worthwhile to send a copy of the mag. to each Australian Public Library, all other technical publications do. Just think of it, my monthly publication in the English language, as she is writing, might yet grace the shelves of all Australian Public Libraries.

Having made a 1953 resolution not to write too much copy for the magazine, ho-hum, and not to be too human, I must confess that, however, many thanks for all the cards and letters, coarse and refined, received from everybody, and I can only say with traditional modesty— I get as much fun out of writing the notes as apparently the readers do. My cup of happiness is brim-full at the moment, because nobody in VK3 could find any Pansy Xmas Cards to send in retaliation. Between you and I, fellows, my stocks are getting very low over here. Can anybody help? 73, de 5PS—Pansy to you.

Repairs to Receivers, Transmitters; Construction and Testing; T.V. Alignment; Low Noise Xtal Conv., any frequency, £18/10/0 plus tax.

ECCLESTON ELECTRONICS
146a Cotham Road, Kew, Vic. WY 3777.

D.C. CONVERTER TRANSFORMERS

Miniature toroidal transformers for transistor d.c. to d.c. converters. Fully encapsulated in epoxy resin. Suitable for horizontal or upright mounting. Voltage doubler circuit.

12v. in, 300v. 100 mA. out 24
12v. in, 300v. 200 mA. out 25

Other voltages up to 350 volts output supplied to order.

400v. silicon rectifiers 8/11

Above prices subject to sales tax. Carriage free.

ELIZABETH ELECTRONICS
P.O. Box 7, Elizabeth, South Aus.

WESTERN AUSTRALIA

Following my predictions recently in regard to what became known as "Games" I can only say "I told you so!" The moment of crisis occurred at about 4 p.m. on Dec. 1 and the party was declared out of danger. In fact by the time Sunday morning came there was practically no signs of the fever left, and the 50,000 people, who had been so violently affected the day before, found they had nothing to do except be a little sad that the whole thing was now over and they must now commence a long week home to their parts of the world, not to mention various parts of Australia.

The biggest thing that I am sorry about is the fact that my report was in on 9 a.m. Sat. 1st Dec. till 11.30 a.m. that night and apparently was too much for it and at the time of writing still hasn't been fixed. Anybody who had a good tv. technician in this area? Alternatively, anybody want to buy the 16 pieces I have spread over the lounge room floor? What's that? No! You can't have that piece there. That's the neighbour's daughter. She only came in to watch the Games!

Presumably, my spies are still doing a recovery bit from the Games, for I have had no reports for some time now. At least I presume that is what has happened.

Lance 6LR is having trouble with a pirate. The information has been passed to the right quarters, but all Hams are warned, so if you contact a bloke with the call 6LR and you know it isn't Lance, see if you can pin-point the signal.

Heard an interesting tape recording recently. Bill 6BZ has a taped some of the 6 mX break-throughs recently. VK3, 4, 5 on the ether and even 9AU. Fine bit, chaps. Keep the good work going.

Still on 6, believe that Brian 5VV at Geraldton has been in contact with Bob 6BR every a.m. lately, although sometimes has been down to c.w. copy, contact has still been maintained. Brian 5VV has also been in contact with Don 6HK, from 2 to 6 mX. What about a note about the activities either or both Brian and Don? I'll be glad to hear.

Another Brian 6ZDE has been doing some heavy iron work on a choke recently. The core is about 1/4 cubic foot and Brian hopes to convert this to a Ham band choke which by the use of silicon rectifiers, will give 1/4 an amp at 3, 6, 9 or 12 hundred volts. What! All that meat and no potatoes? How about an article on the job, Brian? If you have finished, Brian's cohort, Bob 6ZDP says he hasn't been doing anything, but I suspect he's just waiting for the 5V of the 6Z to be finished.

Dennis 6AW says he hasn't got an antenna for the band, 160, 80, 40, 20, 15 or 10, but he is going to have a beauty on 6 and an even better one on 2 with a 2 element, 6 over 6 waving about on his extended tower. So watch out for the big signal.

Great excitement at the QTH of Allyn 6ZDM recently. Allyn's XYL presented him with a lady Junior officer. Allyn is a 1st Lt. and you'd have thought he'd done the whole job himself. All the best to both XYL and babe, Allyn, and try and keep your wife and other people can produce daughters too, you know.

By the way, there is a job coming up in the new year for somebody. You may have heard of the efforts made in the other States to organise the young people who are showing an interest in Ham Radio. Well, the same sort of thing is badly needed in this State. So give it some thought, and if you are in preserving the craft, if nothing else. Hop in with your offer to help the youth of our State.

Talking about new jobs, reminds me, Council is hoping to improve the Bulletin presentation in 1954. So you literary types are required for the magazine committee.

As it is 1953 by the time you read this, may I extend the compliments of the season to you from all members of Council and all other members of the Division. 73, 6LS.

TASMANIA

The holiday season has produced a very good crop of mobile and fixed portable stations. Noted 7ZB and 7ZC at Snowy Mountains. Ken 7KA on the yacht "Moorina" around the southern coast. Lee 7KC with his recently installed car equipment, motoring soberly around Hobart. Don 7KW (the "Voice of Beca") mobiling nimbly around the Island, Bill 7YY from his country residence, "Checkers" in Davey; myself, unriggered, paid a call on VK2.

We are sorry that our friend, Jim 7JO, has seen fit to uproot his antenna and re-plant it at Launceston, and we confidently expect to hear Launceston on the air much more than hitherto.

Den 7DK and his XYL Verna (the "Den Keeper") have bought a house in Launceston. We believe they moved on 25th Jan. This should ensure that the Launceston air is now well frequented.

We in Hobart were delighted to see again Brian 7ZBE back from passing his training course in VK3, in preparation for a year of cold feet and icicles on his nose when he is deported to Davis Base in Antarctica where he will be operating under the call sign VK0BE. (Any similarity to civil dignities bestowed on Royal occasions is purely coincidental, Brian assures us.)

Charlie 7KS and Max 7MX were both mobilising on the mainland during Dec., playing fox-hunts on a large scale, to judge from the way they chased each other about.

Andy 3UJ was a visitor to our shores over Christmas and his 15w. was heard pumping out a good signal. 73, 7ZZ.

HAMADS

Minimum 5/-, for thirty words.

Extra words, 2d. each.

Advertisements under this heading will only be accepted from Institute Members who desire to dispose of equipment which is their own personal property. Copy must be received at P.O. Box 38, East Melbourne, C.T. Vic., by 8th of the month, and remittance should accompany the advertisement. Call signs are now permitted in Hamads. Dealers' advertisements not accepted in this column.

FOR SALE: Hammarland HQ180E general coverage Receiver, suitable 115/240V 50/60 cycle supply. 540 Kc. to 30 Mc. with separate bandspread dial on Ham bands. Latest of its type by Hammarland, triple conversion, xtal controlled osc., xtal filter i.f., 100 Kc. xtal marker, s.s.b. upper and lower s.b. and a.m., 0.5, 1, 2, 3 Kc. selectivity, fast attach with selectable delay on a.v.c., adjustable slot filter, 18 tubes. Highly sensitive DX receiver in top notch condition, cost owner over £400 to build. Sell £280 cash. VK2AAK, A. G. Swinton, C/o. P.O. Kulnura, N.S.W.

FOR SALE: One Earnshaw Electronics Pathfinder S.s.b. phasing type exciter, vox, 80 and 20 metre operation, provision for other bands if required. Price, less tubes, £55. VK3HL, Callawadda, Vic.

SELL: Collins KWM1 S.s.b. Transceiver, perfect condition. Best offer. VK3SK, Bob Slutzkin, 8 Lynedoch Ave. S13, Vic. Phone LB 1861.

SELL: Shielded ignition harness for Volkswagen c/w. commercial shielded plugs, shielded distributor cap, coil with built-in coaxial feed-through capacitor, all shielded leads. Hardly used, plugs, etc., as new. £13. VK3WK, Bill Bell, Staywood Park, Wangoom, Vic.

SELL: 100 watt Tx, Geloso V.f.o., in steel cabinet, modulator class B 807s, plus power supplies, £50. Transceiver ATR4B, £5. Geloso G209 Rx, £130. Full particulars from M. O. Bested, VK2ABE, Box 446, Griffith, N.S.W. Phone 560.

TWO Type 122 Transceivers, with power supplies, microphone and headphones. Good condition. Sell for £35 or consider swap for 2 metre gear other than 522 equipment. VK2YN, 7 Manning St, Narrabri, N.S.W.

IT'S NEW! IT'S NEW!

AMATEUR RADIO HANDBOOK

BY R.S.G.B.

Price 56/3 and 2/6 postage

This book provides a first class course of instruction for the intending Amateur Operator and a gold mine of reference for those already experienced

A MUST FOR ALL ENTHUSIASTS!

AVAILABLE NOW FROM:—

McGILL'S AUTHORISED NEWSAGENCY

Established 1860.

183-185 ELIZABETH STREET, MELBOURNE, C.1, VIC.

"The Post Office is opposite"

Phones: 60-1475-6-7



UNIVERSAL SOUND

A Product of Italy

Model 601 is a Dynamic Unidirectional (Cardioid) Microphone for studios, music and public address, strongly built and famous for quality.

Output: —54 db. (1 volt p/microbar).
Response: 50-12,000 c.p.s. unidirectional.
Impedance: 25,000 ohms, easily stepped down to 250 ohms.
High or low impedance selection.
Dimensions overall: 60 x 60 x 155 mm.
(2-3/8" x 2-3/8" x 6-1/8").


Low frequency change switch for use when speaking.

DYNAMIC CARDIOID MICROPHONE Model 601

Free of amplitude, phase and harmonic distortions. High and low impedance. It offers an additional discrimination factor with a difference of 18 db. from front to back.

On-off switch on handle.
Detachable connector.

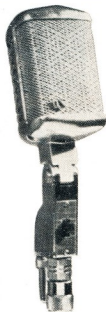Retail Price: £25/14/0
Plus Sales Tax £2/9/0




Marketed by **ZEPHYR PRODUCTS PTY. LTD.**

58 HIGH STREET, GLEN IRIS, S.E.6, VICTORIA

Phones: 25-1300, 25-4556

NOW MADE IN AUSTRALIA

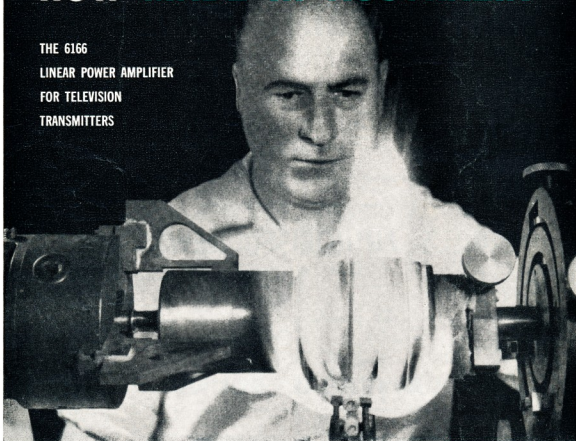THE 6166
LINEAR POWER AMPLIFIER
FOR TELEVISION
TRANSMITTERS



BY AMALGAMATED WIRELESS VALVE CO. PTY. LTD.

AWV proudly announce that the 6166 transmitting beam power tetrode is now being manufactured at its Rydalmere, N.S.W., factory and is available ex stock.

Rated for 10Kw plate dissipation at frequencies up to 216 Mc, the 6166 will deliver 12Kw of synchronising-level power at 216 Mc (USA system) as a class B linear amplifier in television service.

The 6166 is of modern construction and features a coaxial electrode structure designed for use with rf circuits of the coaxial cylinder type which have high efficiency at the operating frequencies of the 6166. The structurally strong conical supports for grid No. 1 and grid No. 2 serve to cool these grids and minimize inductance.

